

**Instructor:**

Asst. Prof. Onur Kurt

**Student Name:**

**ID:**

**Date:**

**ITU**

**EHB 211E: Basics of Electrical Circuits (Fall 2020)**

**Homework 3**

**Grading Policy:**


- You must upload your homework assignment to Ninova before its due date. Late homework will not be accepted/graded.
- Homework should be written clearly and legibly. Your answers should show step-by-step solution of each question. Messy and illegible homework may not be graded.
- You must not ask for answers directly from any aide.
- Academic dishonesty is unacceptable. Plagiarism and cheating on the homework assignment will result in a zero grade.

**Question 1-** The circuit shown below utilizes an ideal op amp.

a-) Find  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_L$ , and  $V_X$ .

b-) If  $V_0$  is not to be lower than  $-13$  V, find the maximum allowed value for  $R_L$ .

c-) If  $R_L$  is varied in the range  $100\ \Omega$  to  $1\text{ k}\Omega$ , what is the corresponding change in  $I_L$  and in  $V_0$ ?

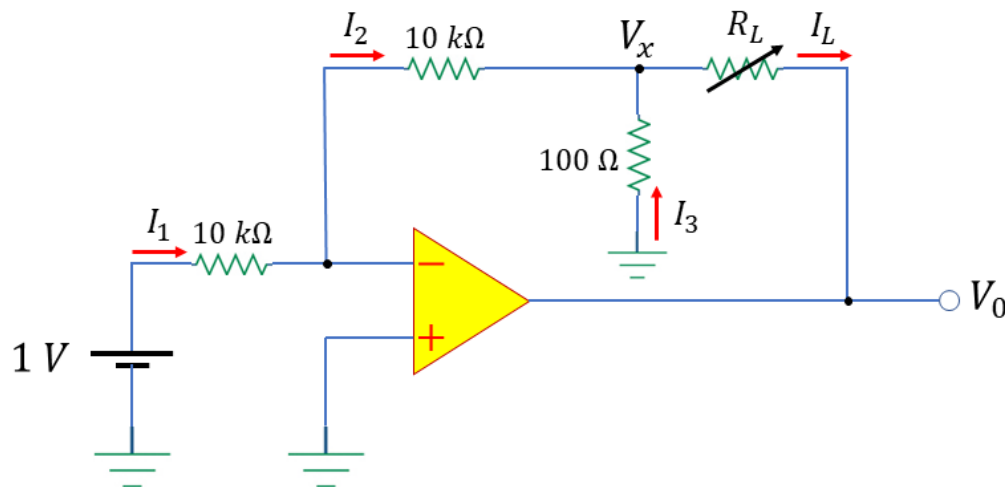


**Question 2-** For the op amp circuit shown below, find  $v_0$  in terms of the input voltages  $v_1$  and  $v_2$ . Assume the op amp is ideal.


For

$$v_1 = 10 \sin(2\pi \times 60t) - 0.1 \sin(2\pi \times 1000t), \text{ volts}$$

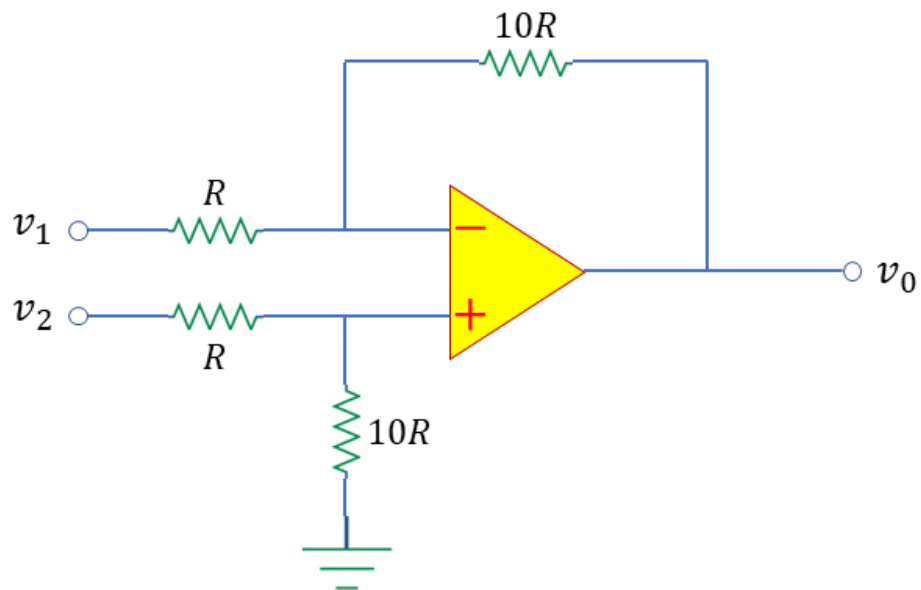
$$v_2 = 10 \sin(2\pi \times 60t) + 0.1 \sin(2\pi \times 1000t), \text{ volts}$$



**Question 3-)** For the op amp circuit shown below, let  $v_s = 10\text{ V}$ , and choose proper values for  $R_a$ ,  $R_b$ , and  $R_c$  to ensure an output voltage  $v_o = 5\text{ V}$ . Assume the op amps are ideal.

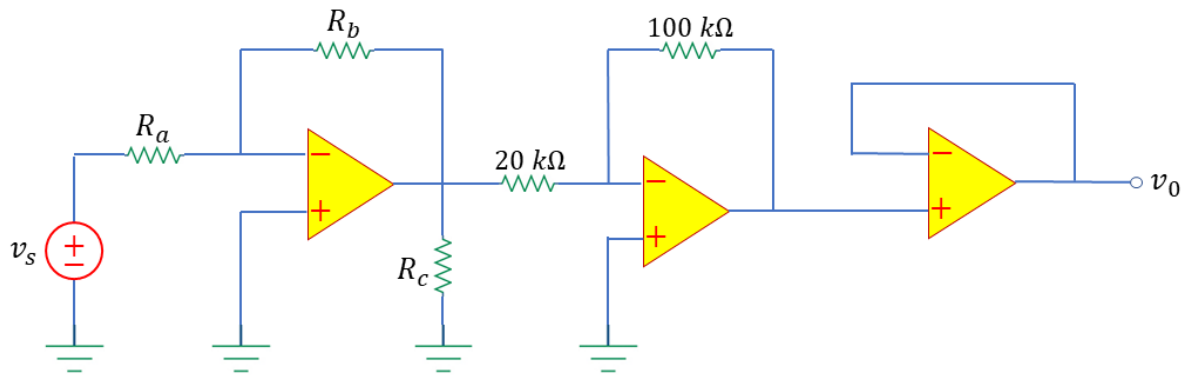

**Question 4-** For the op amp circuit shown below, find the value of  $v_o$ .

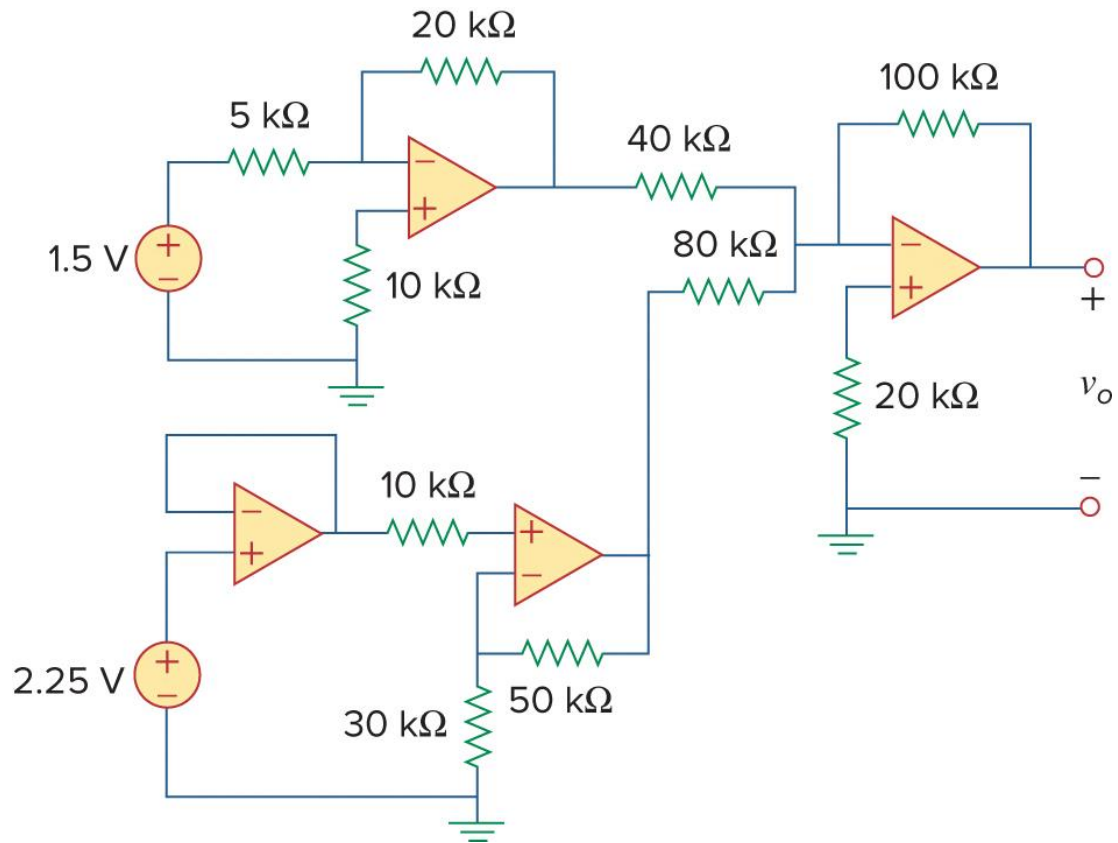

**Question 5-** For the op amp circuit shown below, find the value of  $v_o$  using PSpice.

