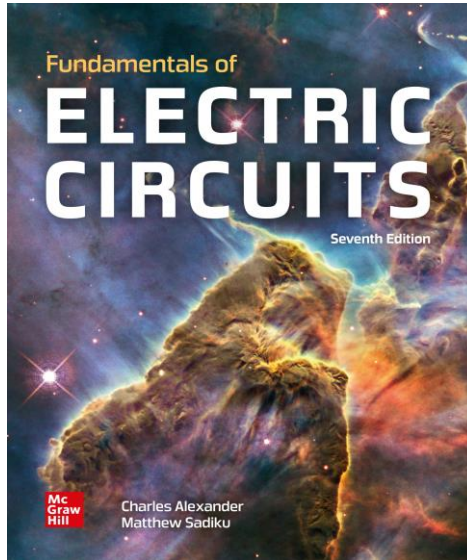


EHB 211E

Basics of Electrical Circuits

Asst. Prof. Onur Kurt

First-Order Circuits



- Study two types of simple circuits:
 - Circuit: a resistor and capacitor \longrightarrow RC circuit
 - Circuit: a resistor and inductor \longrightarrow RL circuit
- Analysis of RC and RL circuits by applying Kirchhoff's law (KCL & KVL)
- Applying Kirchhoff's law to pure resistive circuits: Algebraic equations
- Applying Kirchhoff's law to RC & RL circuits: Differential equations
- Differential equations from RC & RL circuits are of the first-order circuit. Hence, the circuit known as first-order circuits.
- First-order circuit is characterized by a first-order differential equation.
- Two ways to excite these circuits:
 - Initial conditions of the storage elements (source-free circuit). No independent element and energy initially stored in the capacitive and inductive element. They may have dependent sources.
 - Exciting first-order circuits by independent sources.

The Source-Free RC Circuit

- Source-free RC circuit: dc source is suddenly disconnected.
- Energy already stored in the capacitor and released to the resistors.
- Objective: determine the circuit response
- Voltage across capacitor $v(t)$
- Capacitor is initially charged and assume $t = 0$, the initial voltage is $v(0) = V_0$
- Energy stored in the capacitor:


$$w(0) = \frac{1}{2} C (V_0)^2 \text{ at } t = 0 \longrightarrow \text{Initial energy stored}$$

- Apply KCL to the top node: $i_C + i_R = 0$

- By definition: $i_C = C \frac{dv}{dt}$ and $i_R = \frac{v}{R}$

$$C \frac{dv}{dt} + \frac{v}{R} = 0 \Rightarrow \frac{dv}{dt} + \frac{v}{RC} = 0 \longrightarrow \text{First-order differential equation}$$

A source-free RC circuit

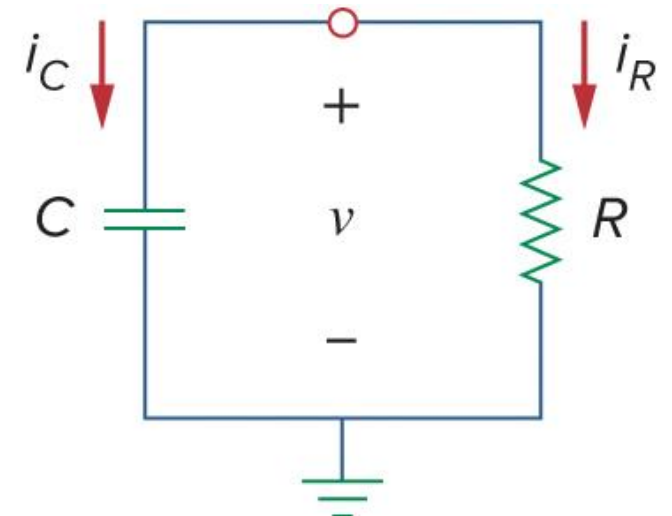

The Source-Free RC Circuit

$$\frac{dv}{dt} + \frac{v}{RC} = 0 \quad \longrightarrow \quad \frac{dv}{dt} = -\frac{v}{RC} \Rightarrow \frac{dv}{v} = -\frac{1}{RC} dt \quad \longrightarrow \quad \text{Integrate both sides of this equation}$$

$$\int \frac{dv}{v} = -\frac{1}{RC} \int dt \quad \longrightarrow \quad \ln v = -\frac{t}{RC} + A \quad \text{A is the constant of the integral part}$$

$$\log_e v = -\frac{t}{RC} + A \quad \longrightarrow \quad v(t) = e^{-\frac{t}{RC} + A} \quad \longrightarrow \quad v(t) = e^{-\frac{t}{RC}} \overset{\substack{\text{Constant} \\ \downarrow}}{\boxed{e^A}}$$

- Let's call $e^A = V_0$ because at $t = 0$, $v(0) = e^0 e^A = V_0$

$$v(t) = V_0 e^{-\frac{t}{RC}}$$

The Source-Free RC Circuit

$v(t) = V_0 e^{-\frac{t}{RC}}$ \longrightarrow Voltage response of RC circuit is exponential decay of the initial voltage

- When $t = 0$, $v(t) = V_0$ (voltage across capacitor is initial voltage).
- When $t = \infty$, $e^{-\frac{\infty}{RC}}$ approaches zero and $v(t) = 0$ (discharging over certain amount of time).
- The response is due to initial voltage not due to some external voltage or current source. Hence, it is called natural response of the circuit.
- Natural response of a circuit refers to the behavior of the circuit itself, with no external sources of excitation.


The Source-Free RC Circuit

- Rapid decrease of voltage can be expressed in terms of the time constant τ , unit is second.
- Time constant τ of a circuit is the time required for the response to decay to a factor of $1/e$ or 36.8 percent of its initial value.

$$\text{At } t = \tau, \quad v(t) = V_0 e^{-\frac{t}{RC}} \longrightarrow V_0 e^{-\frac{\tau}{RC}} = V_0 e^{-1} \Rightarrow \frac{\tau}{RC} = 1 \Rightarrow \tau = RC$$

$\tau = RC$ Time constant of capacitor

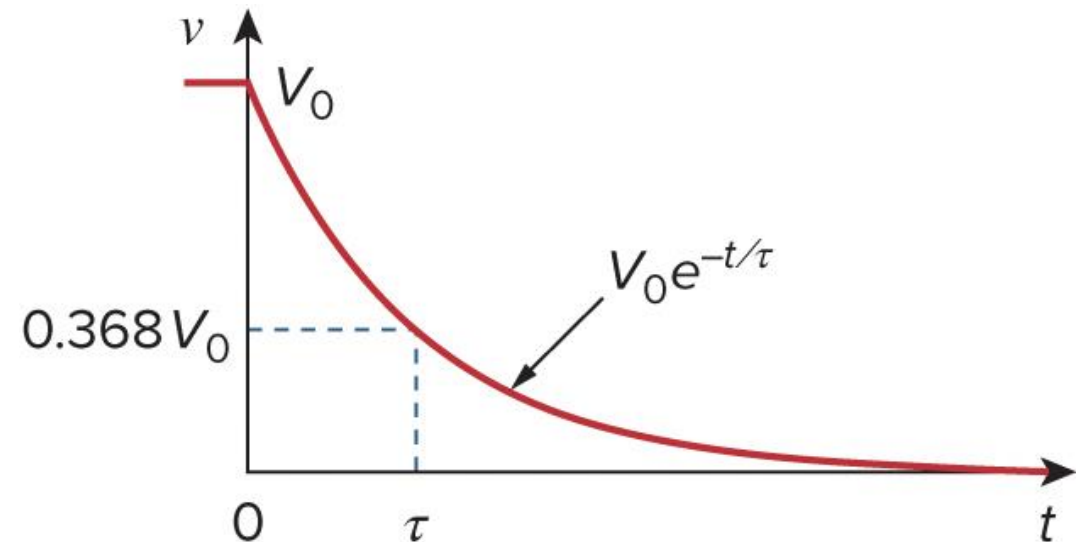$v(t) = V_0 e^{-\frac{t}{\tau}}$ Voltage response of the RC circuit



The Source-Free RC Circuit

- Table shows how the value of $v(t)/V_0$ changes when time t increases
- After 5τ , $v(t)$ is less than 1% of V_0 . It takes approximately 5τ for the circuit reach its final state or steady state (Capacitor is fully discharged after 5τ).
- Smaller the time constant (τ), more rapidly voltage decreases, i.e., faster response.

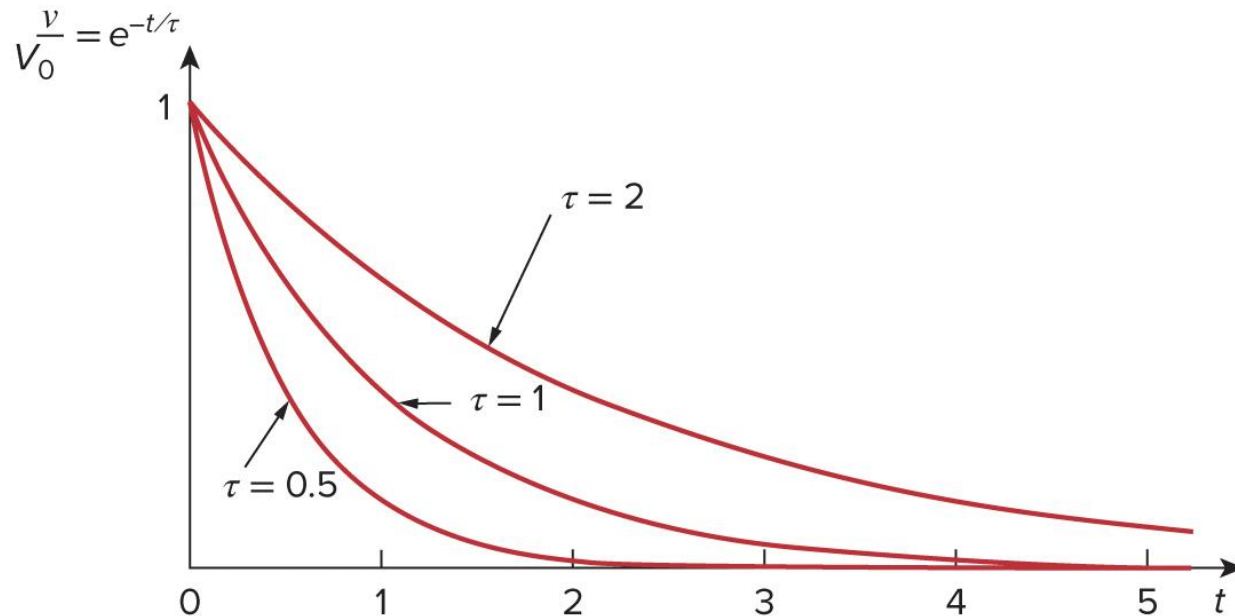


TABLE 7.1

Values of $v(t)/V_0 = e^{-t/\tau}$.

t	$v(t)/V_0$
τ	0.36788
2τ	0.13534
3τ	0.04979
4τ	0.01832
5τ	0.00674

The Source-Free RC Circuit

- Using Ohm's law, the current $i_R(t)$ is expressed as:

$$i_R(t) = \frac{v(t)}{R} = \frac{V_0}{R} e^{-\frac{t}{\tau}}$$

- Power dissipated in the resistor:

$$p(t) = vi_R \longrightarrow p(t) = \left(V_0 e^{-\frac{t}{\tau}}\right) \left(\frac{V_0}{R} e^{-\frac{t}{\tau}}\right) \longrightarrow p(t) = \frac{(V_0)^2}{R} e^{-\frac{2t}{\tau}}$$

- Energy absorbed by the resistor:

$$p = \frac{w}{t} \Rightarrow w = pt \longrightarrow \text{Derivation of both sides of this equation} \longrightarrow dw = p dt \longrightarrow \text{Integrate both sides}$$

$$\int dw = \int p dt \longrightarrow w_R(t) = \int_0^t p(t) dt \Rightarrow w_R(t) = \int_0^t \frac{(V_0)^2}{R} e^{-\frac{2t}{\tau}} dt = -\frac{\tau(V_0)^2}{2R} e^{-\frac{2t}{\tau}} \Bigg|_0^t, \tau = RC$$

$$= -\frac{RC(V_0)^2}{2R} e^{-\frac{2t}{\tau}} \Bigg|_0^t = \frac{1}{2} C(V_0)^2 (1 - e^{-\frac{2t}{\tau}})$$

- When $t = \infty$, $e^{-\frac{2t}{\tau}}$ approaches 0

$$w_C = \frac{1}{2} C(V_0)^2$$

Example 1

For the circuit shown below, let $v_C(0) = 15 \text{ V}$. Find v_C , v_x , and i_x for $t > 0$.

Solution:



$$R_{\text{eq}} = \frac{20 \times 5}{20 + 5} = 4 \Omega$$

$$\tau = R_{\text{eq}}C = 4(0.1) = 0.4 \text{ s}$$

$$v = v(0)e^{-t/\tau} = 15e^{-t/0.4} \text{ V}, \quad v_C = v = 15e^{-2.5t} \text{ V}$$

$$v_x = \frac{12}{12 + 8}v = 0.6(15e^{-2.5t}) = 9e^{-2.5t} \text{ V}$$

$$i_x = \frac{v_x}{12} = 0.75e^{-2.5t} \text{ A}$$

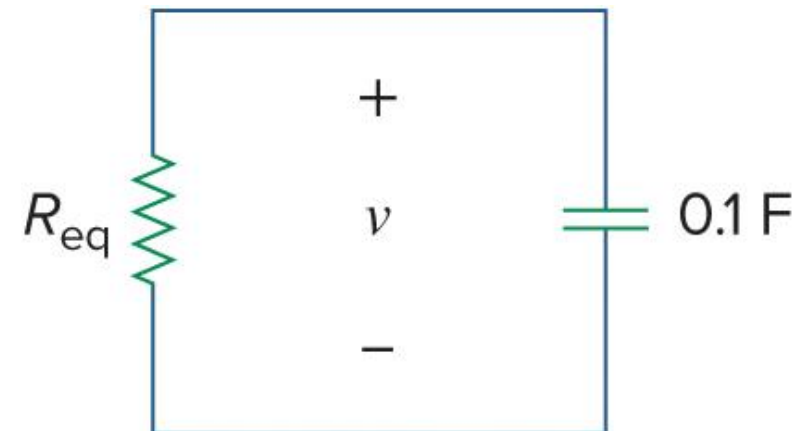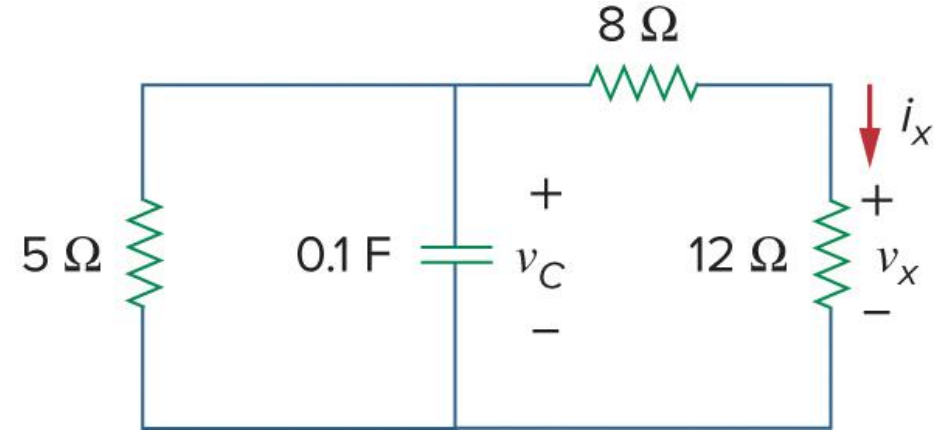

Example 2

The switch in the circuit shown below has been closed for a long time, and it is opened at $t = 0$. Find $v(t)$ for $t > 0$. Calculate the initial energy stored in the capacitor.

Solution:

For $t < 0$ the switch is closed; the capacitor is an open circuit to dc

$$v_C(t) = \frac{9}{9 + 3}(20) = 15 \text{ V}, \quad t < 0$$




Since the voltage across a capacitor cannot change instantaneously, the voltage across the capacitor at $t = 0^-$ is the same at $t = 0$ or

$$v_C(0) = V_0 = 15$$

For $t > 0$ the switch is opened: $R_{eq} = 1 + 9 = 10 \Omega$

$$\tau = R_{eq}C = 10 \times 20 \times 10^{-3} = 0.2 \text{ s} \quad v(t) = v_C(0)e^{-t/\tau} = 15e^{-t/0.2} \text{ V}$$
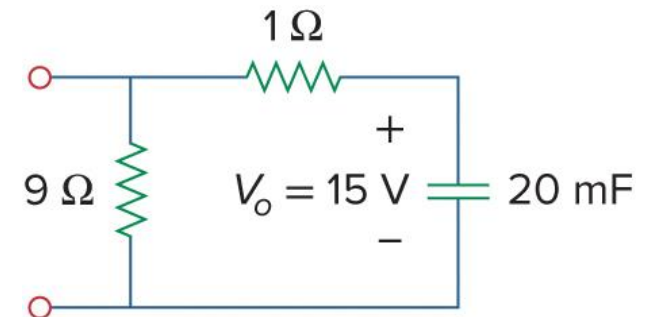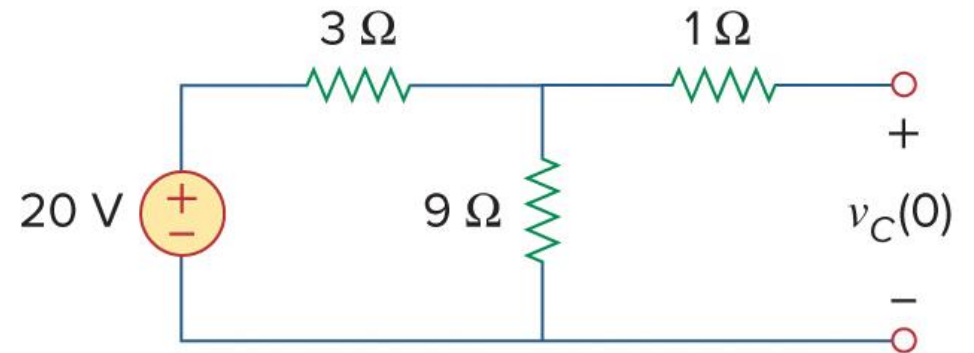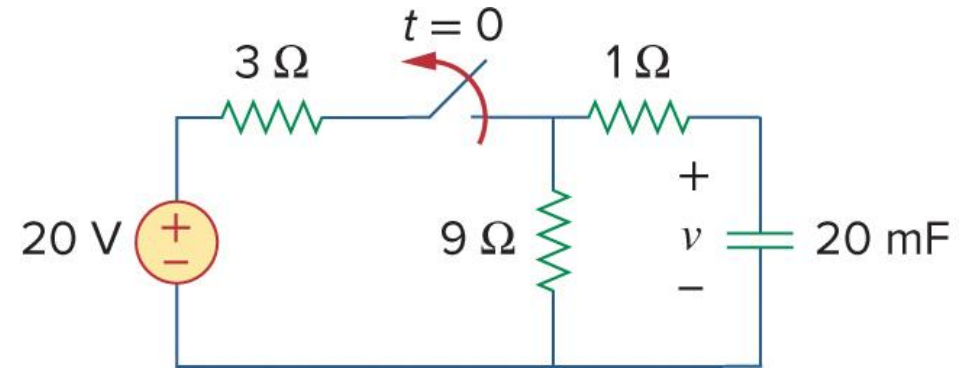
$$v(t) = 15e^{-5t} \text{ V} \quad w_C(0) = \frac{1}{2}Cv_C^2(0) = \frac{1}{2} \times 20 \times 10^{-3} \times 15^2 = 2.25 \text{ J}$$




The Source-Free RL Circuit

- Goal: determine circuit response in RL circuit.
- When $t = 0$, the initial current in the RL circuit (current excite the circuit):

$i(0) = I_0 \longrightarrow$ When $t = 0$, inductor current equal to initial current.

- Initial energy in the inductor:

$$w(0) = \frac{1}{2} L(I_0)^2$$

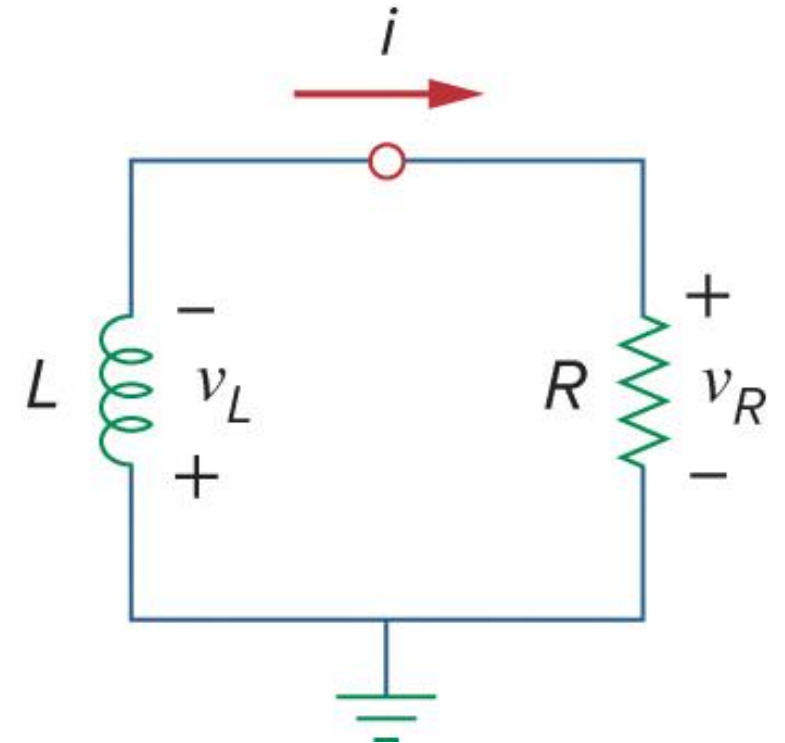

The Source-Free RL Circuit

- Apply KVL to the circuit: $v_L + v_R = 0$, $v_L = L \frac{di}{dt}$

$$L \frac{di}{dt} + iR = 0 \Rightarrow \frac{di}{dt} + \frac{R}{L}i = 0 \Rightarrow \frac{di}{dt} = -\frac{R}{L}i \Rightarrow \frac{di}{i} = -\frac{R}{L}dt \Rightarrow \text{Integrate both sides}$$

$$\int_{I_0}^{i(t)} \frac{di}{i} = -\int_0^t \frac{R}{L}dt \Rightarrow \ln i \Big|_{I_0}^{i(t)} = -\frac{R}{L}t \Big|_0^t$$


$$\ln i - \ln I_0 = -\frac{R}{L}t + 0 \Rightarrow \ln\left(\frac{i}{I_0}\right) = -\frac{Rt}{L}$$

$$\log_e\left(\frac{i}{I_0}\right) = -\frac{Rt}{L} \Rightarrow \frac{i}{I_0} = e^{-\frac{Rt}{L}} \Rightarrow i(t) = I_0 e^{-\frac{Rt}{L}}$$

Natural response of RL circuit is exponential decay of the initial current

$$\tau = \frac{L}{R} \quad \text{Time constant of inductor}$$

$$i(t) = I_0 e^{-\frac{t}{\tau}}$$

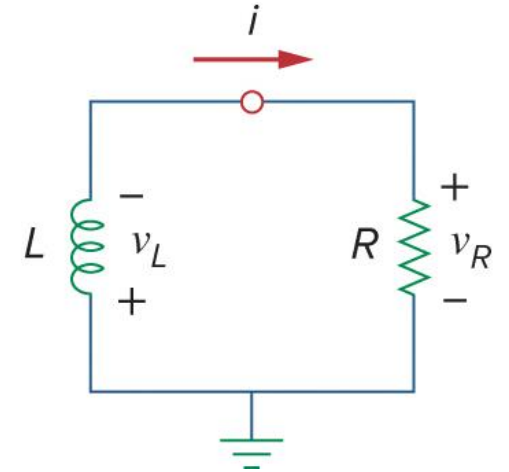

The Source-Free RL Circuit


- When $t < 0$, inductor is charged.
- When $t = 0$, inductor excites the circuit by the stored energy.
- Inductor has an exponential decay due to $e^{-\frac{t}{\tau}}$ term.
- Similar to capacitor, at time $t = \tau$, current through the circuit is 36.8% smaller than initial value.

$$i(t) = I_0 e^{-\frac{t}{\tau}} \Rightarrow i(\tau) = I_0 e^{-\frac{\tau}{\tau}} = \frac{I_0}{e^1} = 0.368 I_0$$

$$v_R(t) = iR \Rightarrow v_R(t) = I_0 R e^{-\frac{t}{\tau}}$$

- Power dissipated in the resistor:
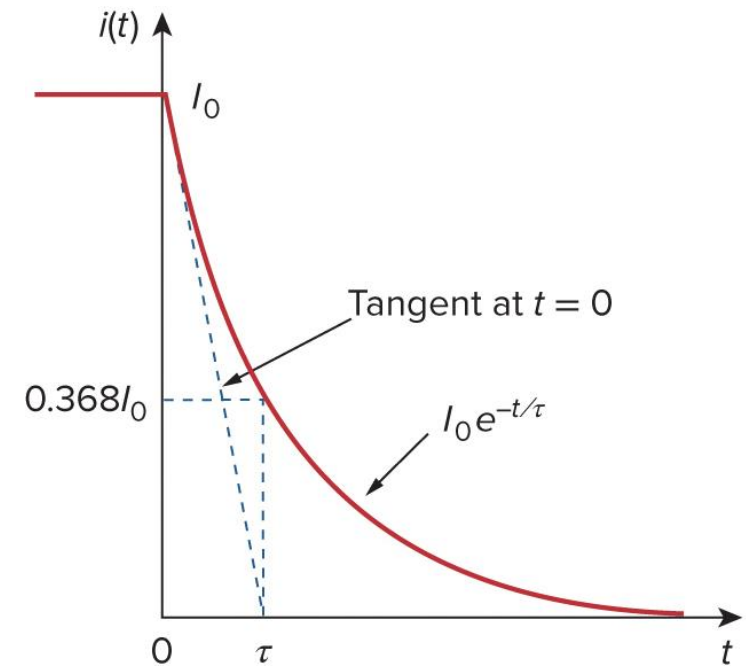
$$p = v_R i \Rightarrow p = (I_0)^2 R e^{-\frac{2t}{\tau}}$$



The Source-Free RL Circuit

- Energy absorbed by the resistor:

$$p = \frac{dw}{dt} \Rightarrow w = pt \quad \Rightarrow \text{Derivation of both sides of this equation} \quad \Rightarrow dw = p dt \quad \Rightarrow \text{Integrate both sides}$$


$$\int dw = \int p dt \quad \Rightarrow w_R(t) = \int_0^t p(t) dt \Rightarrow w_R(t) = \int_0^t (I_0)^2 R e^{-\frac{2t}{\tau}} dt = -\frac{\tau}{2} (I_0)^2 R e^{-\frac{2t}{\tau}} \quad , \quad \tau = \frac{L}{R}$$

$$w_R(t) = -\frac{1}{2} \frac{L}{R} (I_0)^2 R \left(e^{-\frac{2t}{\tau}} \right) \Big|_0^t \quad \Rightarrow w_R(t) = \frac{1}{2} L (I_0)^2 \left(1 - e^{-\frac{2t}{\tau}} \right)$$

- Energy initially stored in the inductor is eventually dissipated by the resistor.
- When $t \rightarrow \infty$, $e^{-\frac{2t}{\tau}} \rightarrow 0$ $w_R(t) = \frac{1}{2} L (I_0)^2 \longrightarrow$ Same as $w_L(0)$ which is the initial energy stored in the inductor.

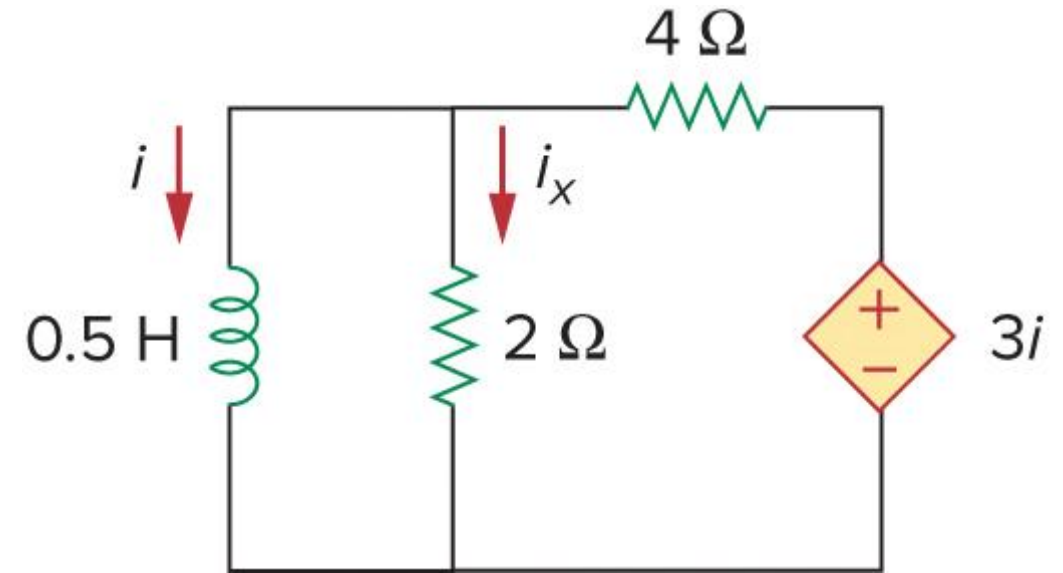Example 3

Assuming that $i(0) = 10$ A, calculate $i(t)$ and $i_x(t)$ in the circuit shown below.



Solution:

This question can be solved in two different ways:

1st: Obtain the equivalent resistance (or Thevenin resistance) at the inductance terminals and then use the current equation

$$i(t) = I_0 e^{-\frac{t}{\tau}}$$

2nd: using KVL to obtain the desired result.

Solution

- **Method 1:** Find equivalent resistance.
- Since the circuit has only dependent source, insert a test voltage source of 1 V at the inductor terminals a-b and find R_{Th} .
- Keep it in mind that we cannot turn off dependent circuit when applying Thevenin theorem.

- To find R_{Th} , we need to find i_0 as $R_{Th} = \frac{v_0}{i_0} = \frac{1}{i_0}$
- Apply KVL both loops:


$$2(i_1 - i_2) + 1 = 0 \Rightarrow i_1 - i_2 = -\frac{1}{2}$$

$$6i_2 - 2i_1 - 3i_1 = 0 \Rightarrow i_2 = \frac{5}{6}i_1$$

$$i_1 = -3 \text{ A}, \quad i_o = -i_1 = 3 \text{ A} \quad R_{eq} = R_{Th} = \frac{v_o}{i_o} = \frac{1}{3} \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{\frac{1}{2}}{\frac{1}{3}} = \frac{3}{2} \text{ s}$$

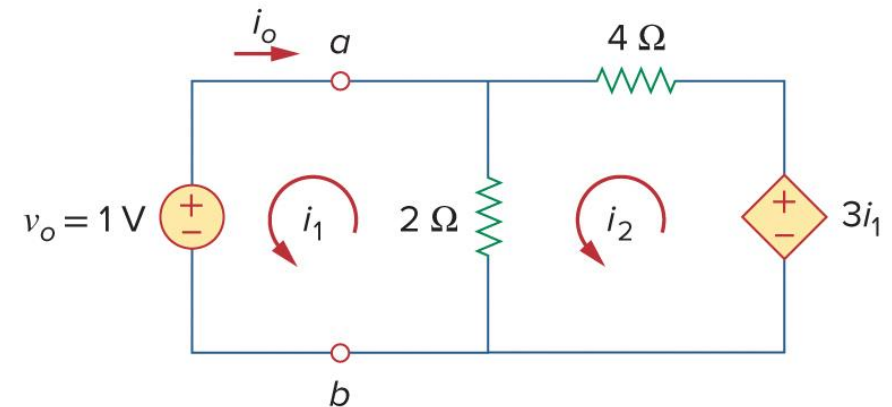
$$i(t) = i(0)e^{-t/\tau} = 10e^{-(2/3)t} \text{ A}, \quad t > 0$$



Solution

- Method 2: apply KVL
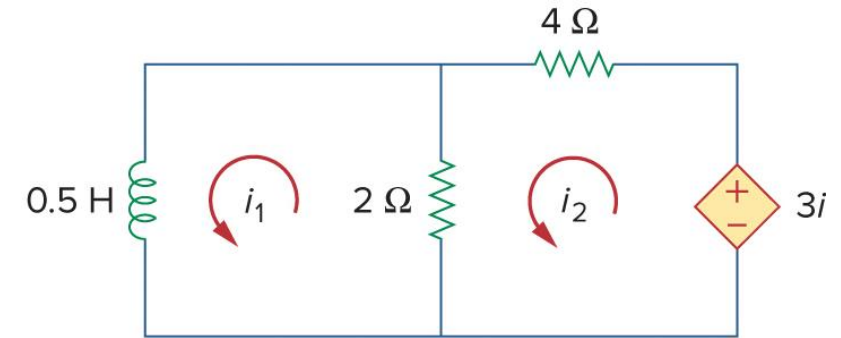
$$\frac{1}{2} \frac{di_1}{dt} + 2(i_1 - i_2) = 0 \quad \text{or} \quad \frac{di_1}{dt} + 4i_1 - 4i_2 = 0$$



For loop 2,

$$6i_2 - 2i_1 - 3i_1 = 0 \quad \Rightarrow \quad i_2 = \frac{5}{6}i_1 \quad \frac{di_1}{dt} + \frac{2}{3}i_1 = 0 \quad \frac{di_1}{i_1} = -\frac{2}{3}dt$$

Since $i_1 = i$, we may replace i_1 with i and integrate: $\ln i \Big|_{i(0)}^{i(t)} = -\frac{2}{3}t \Big|_0^t \quad \text{or} \quad \ln \frac{i(t)}{i(0)} = -\frac{2}{3}t$

$$i(t) = i(0)e^{-(2/3)t} = 10e^{-(2/3)t} \text{ A}, \quad t > 0$$

$$v = L \frac{di}{dt} = 0.5(10) \left(-\frac{2}{3} \right) e^{-(2/3)t} = -\frac{10}{3} e^{-(2/3)t} \text{ V}$$

$$i_x(t) = \frac{v}{2} = -1.6667 e^{-(2/3)t} \text{ A}, \quad t > 0$$

Example 4

The switch in the circuit shown below has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$.

Solution:

For $t < 0$, the switch is closed. This means that inductor is short circuit to dc condition.



$$\frac{4 \times 12}{4 + 12} = 3 \Omega \quad i_1 = \frac{40}{2 + 3} = 8 \text{ A}$$

using current division

$$i(t) = \frac{12}{12 + 4} i_1 = 6 \text{ A}, \quad t < 0$$

Since the current through an inductor cannot change instantaneously,

$$i(0) = i(0^-) = 6 \text{ A}$$

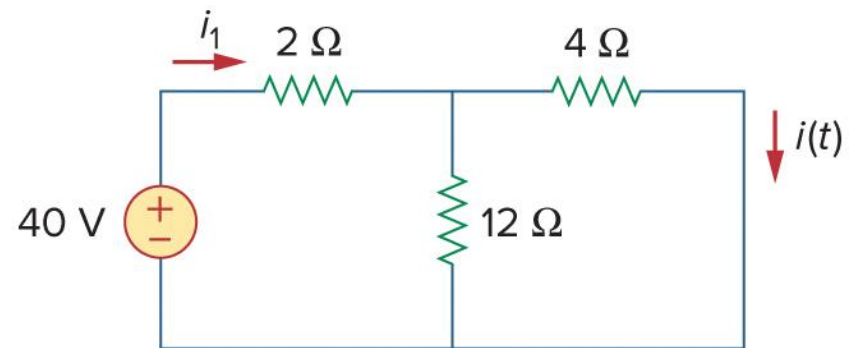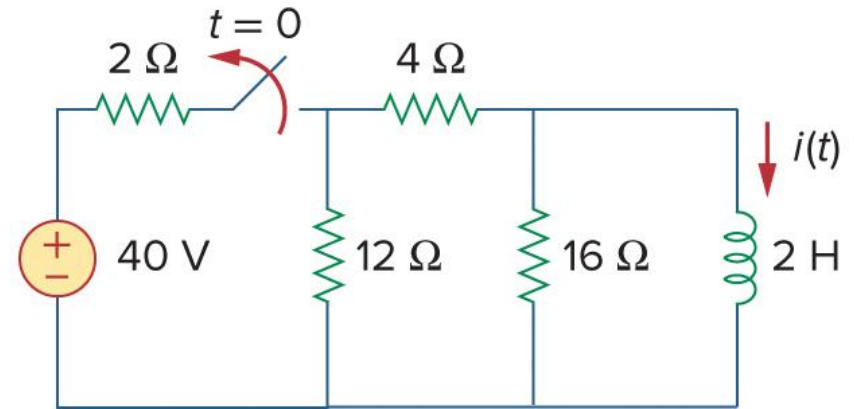

Solution

For $t > 0$, the switch is opened and voltage source is disconnected. This means we have a source-free RL circuit as shown below.



To find $i(t)$, we need to use following equation:

$$i(t) = i(0)e^{-\frac{t}{\tau}}$$

$$R_{eq} = (12 + 4) \parallel 16 = 8 \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2}{8} = \frac{1}{4} \text{ s}$$

$$i(t) = i(0)e^{-t/\tau} = 6e^{-4t} \text{ A}$$

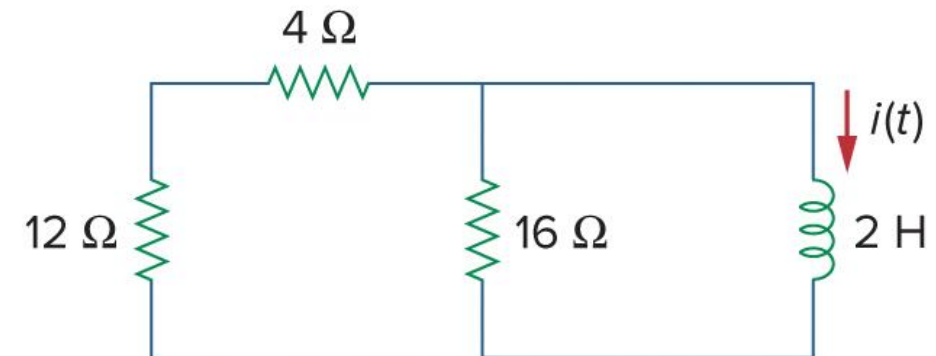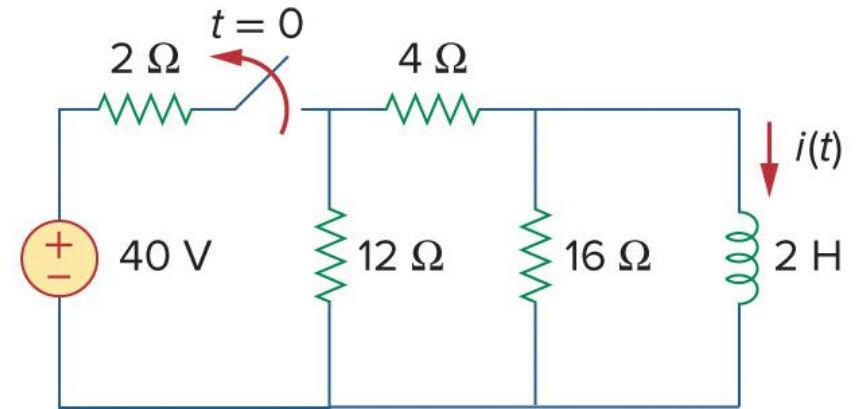

Example 5

In the circuit shown below, find i_0 , v_0 and i for all time, assuming that the switch was open for a long time.


Solution:

For $t < 0$, the switch is opened. Since inductor is short circuit to dc, $6\ \Omega$ resistor is short circuited. $i_0 = 0$

$$i(t) = \frac{10}{2 + 3} = 2\text{ A}, \quad t < 0$$

$$v_o(t) = 3i(t) = 6\text{ V}, \quad t < 0$$
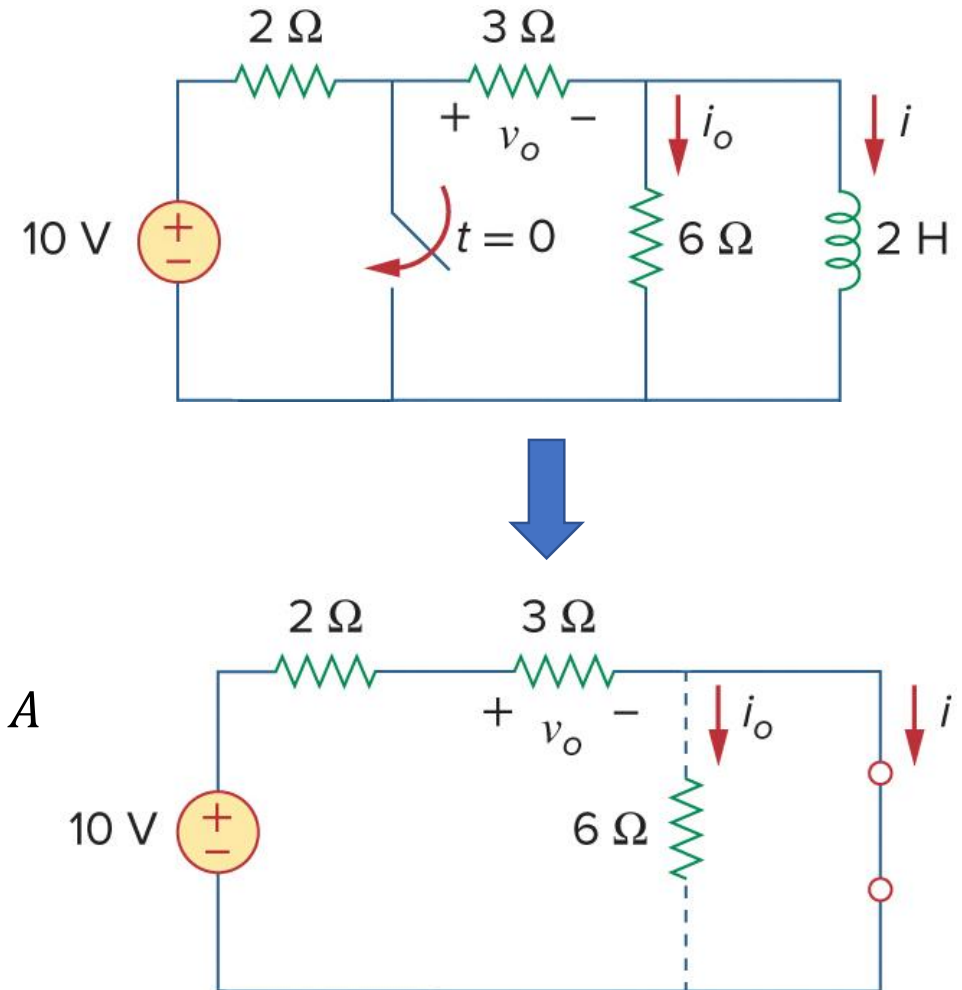
$$i(0) = 2\text{ A because for } t < 0 \text{ \& } t = 0, i(0) = i(0^-) = 2\text{ A}$$



Solution

For $t > 0$, the switch is closed. The voltage is short circuited.

$$R_{Th} = 3 \parallel 6 = 2 \Omega \quad \tau = \frac{L}{R_{Th}} = 1 \text{ s}$$

$$i(t) = i(0)e^{-t/\tau} = 2e^{-t} \text{ A}, \quad t > 0$$

$$v_o(t) = -v_L = -L \frac{di}{dt} = -2(-2e^{-t}) = 4e^{-t} \text{ V}, \quad t > 0$$



$$i_o(t) = \frac{v_L}{6} = -\frac{2}{3}e^{-t} \text{ A}, \quad t > 0$$

Thus, for all time,

$$i_o(t) = \begin{cases} 0 \text{ A}, & t < 0 \\ -\frac{2}{3}e^{-t} \text{ A}, & t > 0 \end{cases} \quad v_o(t) = \begin{cases} 6 \text{ V}, & t < 0 \\ 4e^{-t} \text{ V}, & t > 0 \end{cases}$$

$$i(t) = \begin{cases} 2 \text{ A}, & t < 0 \\ 2e^{-t} \text{ A}, & t \geq 0 \end{cases}$$

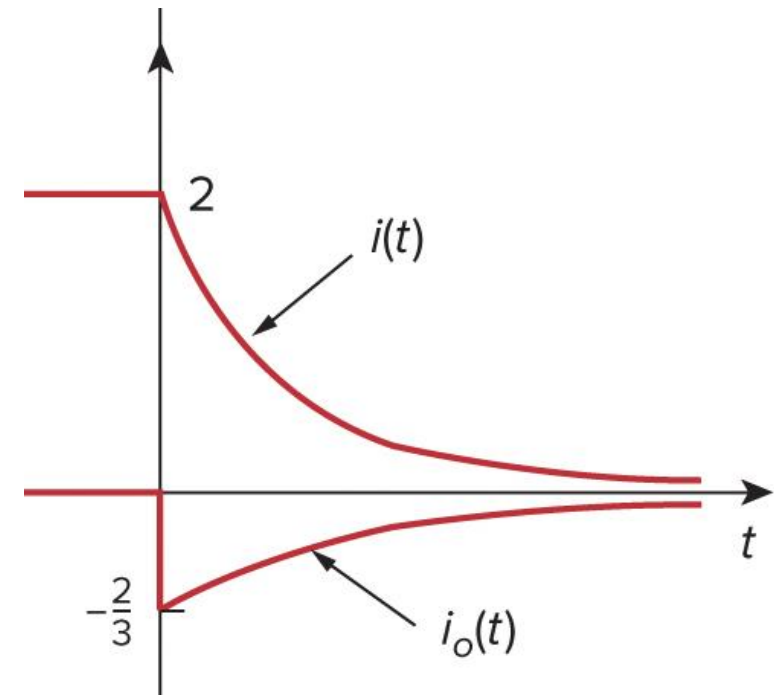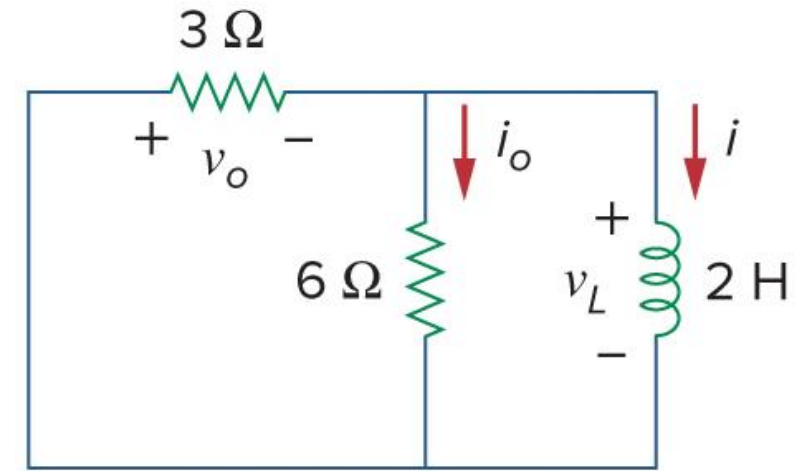From the Graph and expression: the inductor current is continuous at $t=0$ (current through inductor cannot change instantly), while resistor current through 6Ω resistor drop from 0 to $-2/3$ at $t=0$, and voltage across 3Ω resistor from 6 V to 4 V at $t=0$.




Singularity (Switching) Function

- Singularity (aka switching functions): useful for circuit analysis.
- Good approximations to the switching signals that arises in circuit with switching operation.
- Helpful in the neat, compact description of the step response of RC or RL circuit.
- Singularity function: either discontinuous or have discontinuous derivatives.
- Three most widely used singularity functions:
 - ❑ Unit step function
 - ❑ Unit impulse function
 - ❑ Unit ramp function

Unit Step Function

- Unit step function $u(t)$ is 0 for negative value of t and 1 for positive value of t .
- In mathematically,
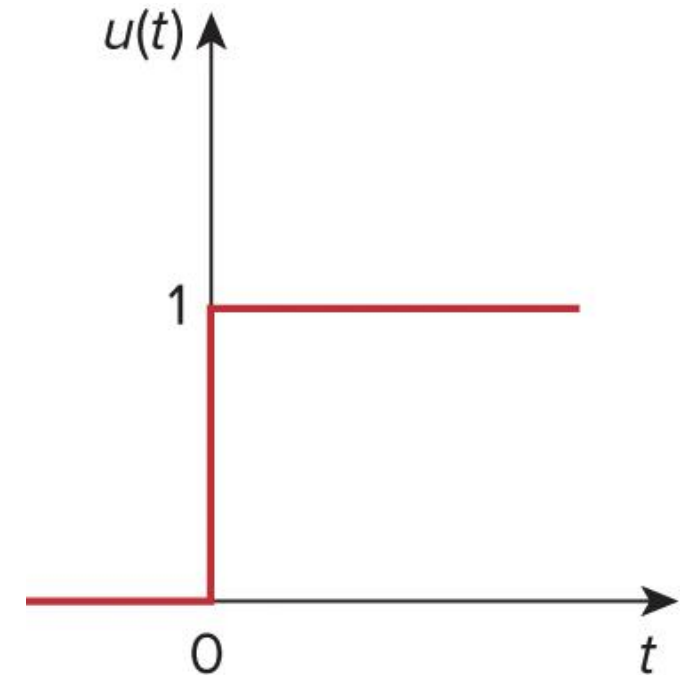
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$




- Unit step function is undefined at $t = 0$ where it changes abruptly from 0 to 1.

Unit Step Function

- Assume that abrupt (sudden) change occurs at $t = t_0$ (where $t_0 > 0$) instead of $t = 0$.

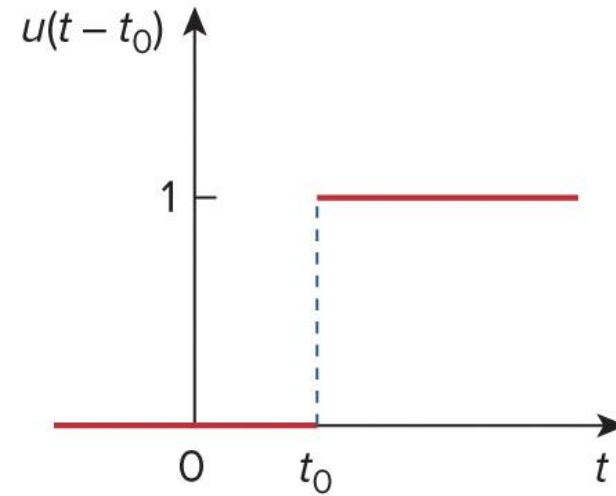
$$u(t - t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$$



$u(t)$ is delayed by t_0 sec

- Assume that abrupt (sudden) change occurs at $t = -t_0$
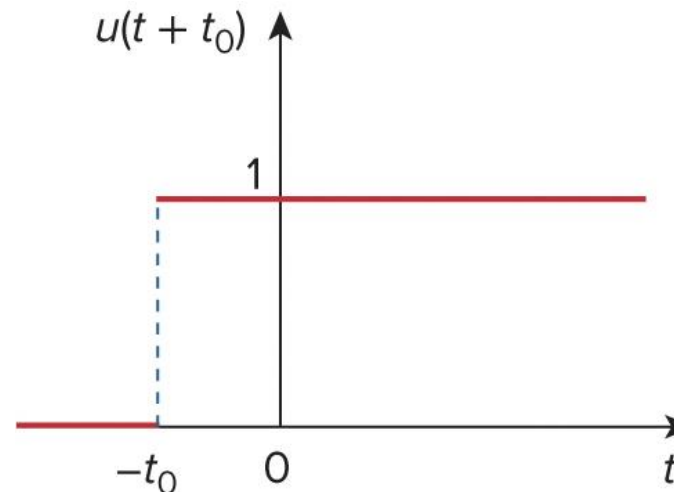
$$u(t + t_0) = \begin{cases} 0 & t < -t_0 \\ 1 & t > -t_0 \end{cases}$$




$u(t)$ is advanced by t_0 sec

Unit Step Function

- An abrupt change in voltage and current can be represented by step function.

$$v(t) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases} \quad \longrightarrow \quad v(t) = V_0(t - t_0)$$

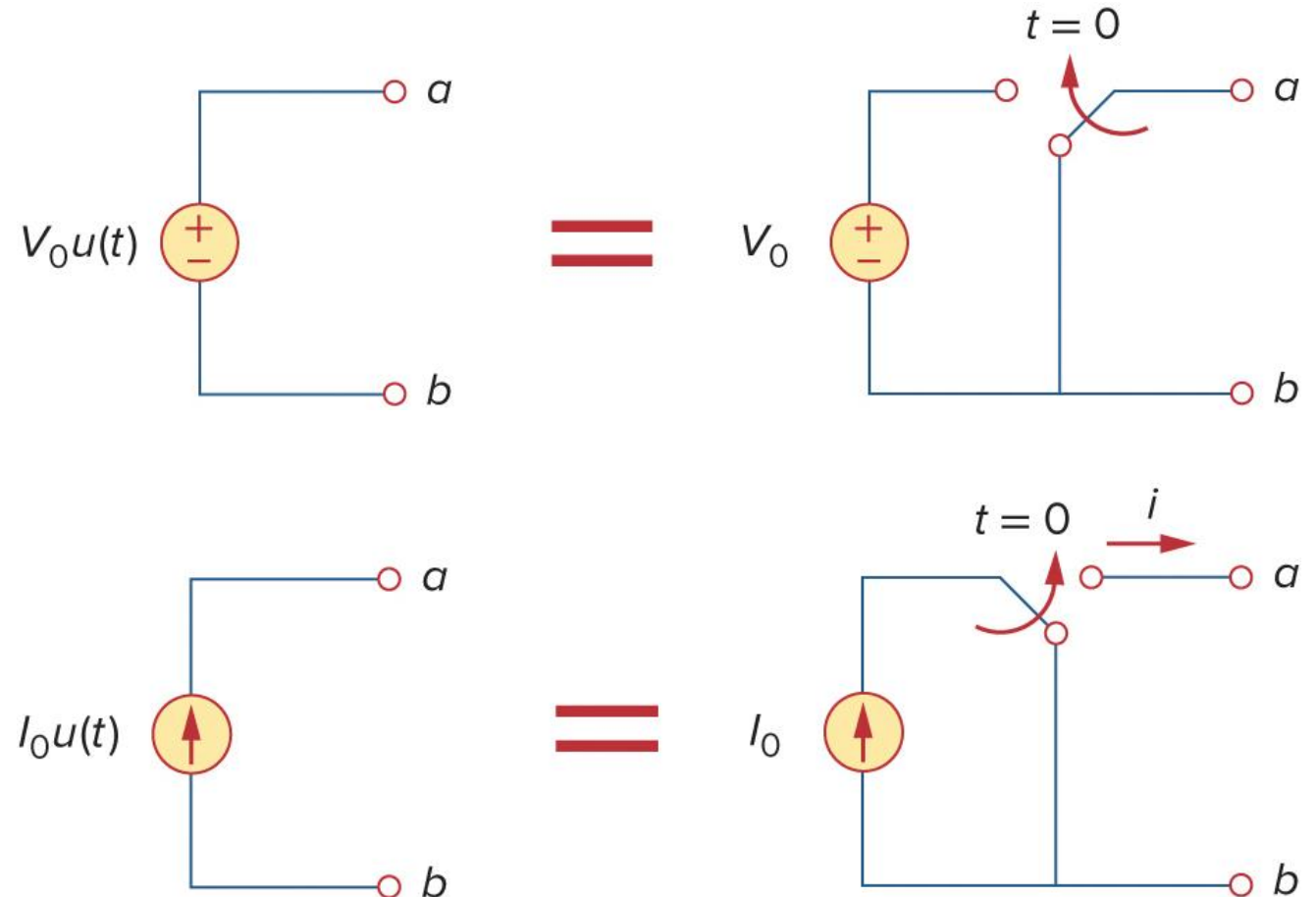
- If $t_0 = 0$, $v(t)$ is simply the step voltage $V_0 u(t)$



Unit Impulse Function

- Derivative of the unit step function $u(t)$ is the unit impulse function (aka delta function) which is represented by $\delta(t)$

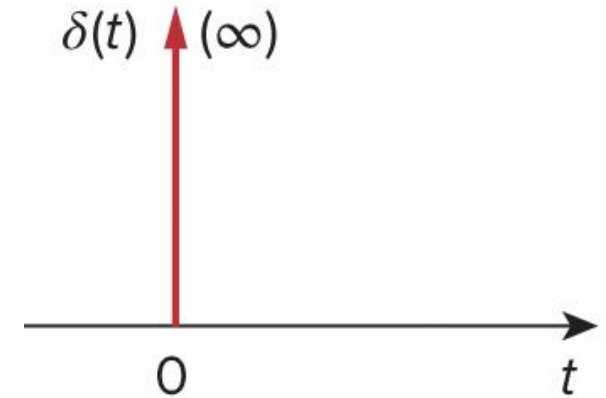
$$\delta(t) = \frac{d}{dt} u(t) = \begin{cases} 0 & t < 0 \\ \text{undefined} & t = 0 \\ 0 & t > 0 \end{cases}$$



- The unit impulse function $\delta(t)$ is zero everywhere except at $t=0$, where it is undefined.
- The unit impulse may be regarded as an applied or resulting shock. It may be visualized as a very short duration pulse of unit area.
- It can be expressed mathematically as:

$$\int_{0^-}^{0^+} \delta(t) dt = 1$$

The strength of the impulse function.

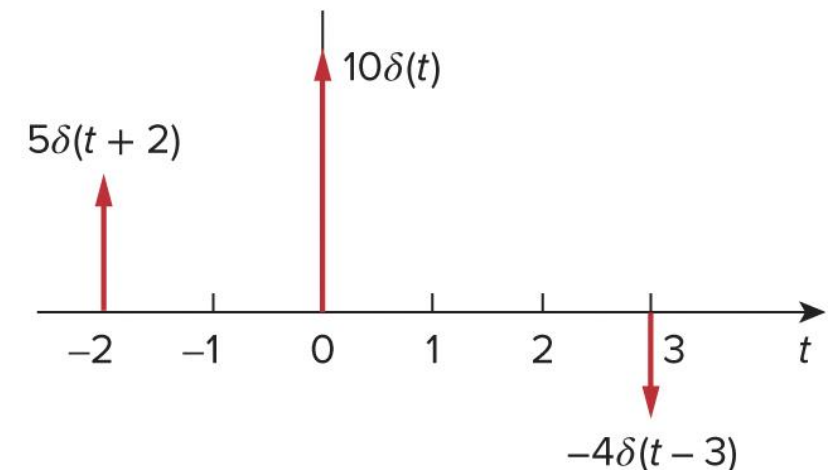


Unit Ramp Function

- Integral of the unit step function $u(t)$ is the unit ramp function $r(t)$:

$$r(t) = \int_{-\infty}^t u(t) dt = u(t) \cdot t$$

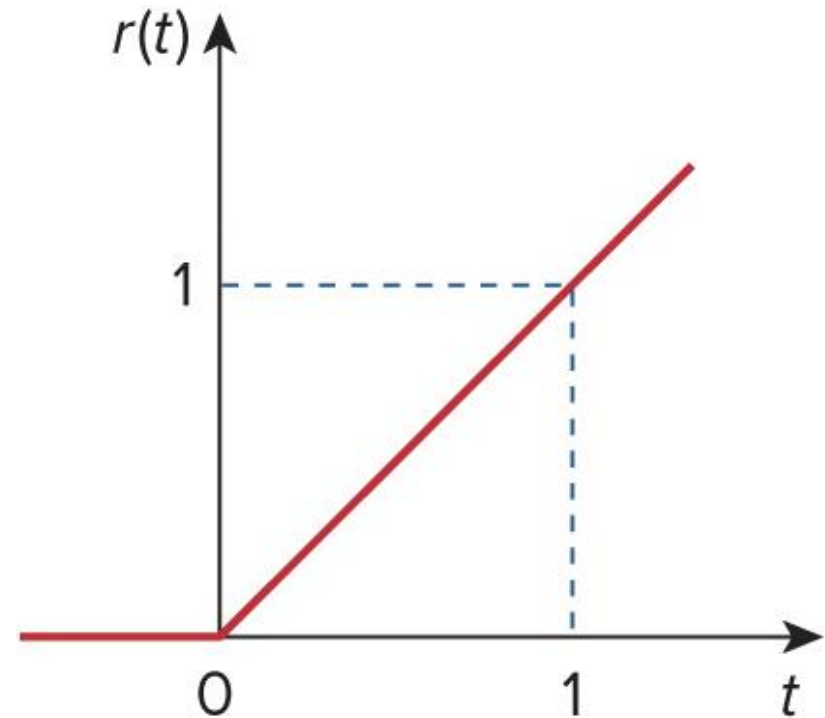
$$r(t) = \begin{cases} 0 & t \leq 0 \\ t & t \geq 0 \end{cases}$$



Unit Ramp Function


- Delayed unit ramp function
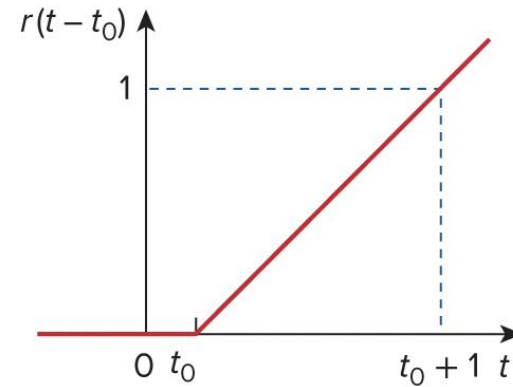
$$r(t - t_0) = \begin{cases} 0 & t \leq t_0 \\ t - t_0 & t \geq t_0 \end{cases}$$



- Advanced unit ramp function
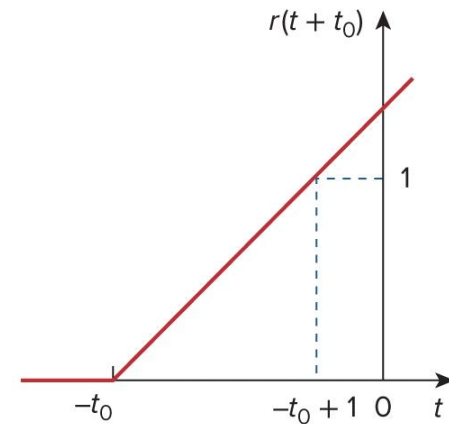
$$r(t + t_0) = \begin{cases} 0 & t \leq -t_0 \\ t + t_0 & t \geq -t_0 \end{cases}$$




- Three singularity functions are related by differentiation or integration:

$$\delta(t) = \frac{du(t)}{dt} \quad u(t) = \frac{dr(t)}{dt}$$

$$u(t) = \int_{-\infty}^t \delta(t) \cdot dt \quad r(t) = \int_{-\infty}^t u(t) \cdot dt$$

Step Response of an RC Circuit

- When the dc source of an RC circuit is suddenly applied, the voltage or current source can be modeled as a step function, and the response is known as a step response.
- The step response is the response of the circuit due to a sudden application of a dc voltage or current source.
- Once the switch is closed, there is a sudden application of dc source. Thus, the circuit replaced by the following circuit (on the right)

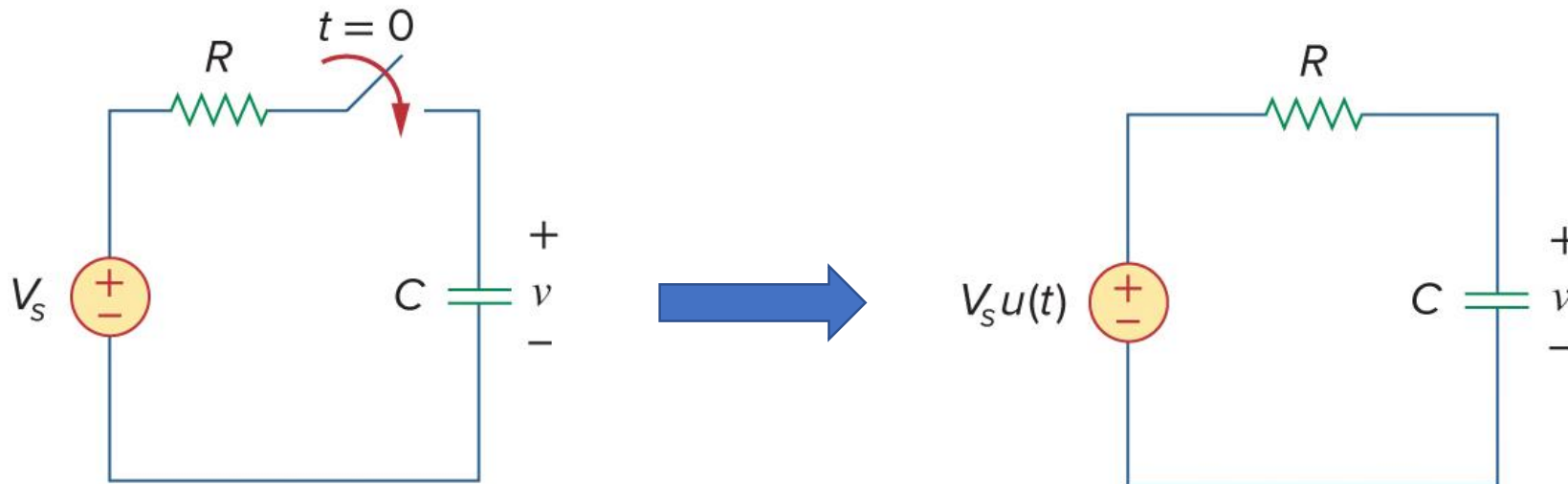

Step Response of an RC Circuit

- Assume V_0 as the initial voltage on the capacitor.
- Voltage of the capacitor cannot change instantaneously,

$$v(0^-) = v(0^+) = V_0 \quad \begin{array}{l} 0^-: \text{just before switching} \\ 0^+: \text{just after switching} \end{array}$$



- Apply KCL: $C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0 \Rightarrow C \frac{dv}{dt} + \frac{v}{R} - \frac{V_s u(t)}{R} = 0$

$$C \frac{dv}{dt} + \frac{v}{R} = \frac{V_s u(t)}{R} \Rightarrow \frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC} u(t) \quad \begin{array}{l} \text{For } t > 0, \text{ unit} \\ \text{step function is 1} \end{array}$$

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC} \Rightarrow \frac{dv}{dt} = -\frac{v - V_s}{RC} \Rightarrow \frac{dv}{v - V_s} = -\frac{dt}{RC} \Rightarrow \text{Integrate}$$

$$\int_{v(0)}^{v(t)} \frac{dv}{v - V_s} = -\int_0^t \frac{1}{RC} dt \Rightarrow \ln(v - V_s) \Big|_{V_0}^{v(t)} = -\frac{t}{RC} \Big|_0^t$$
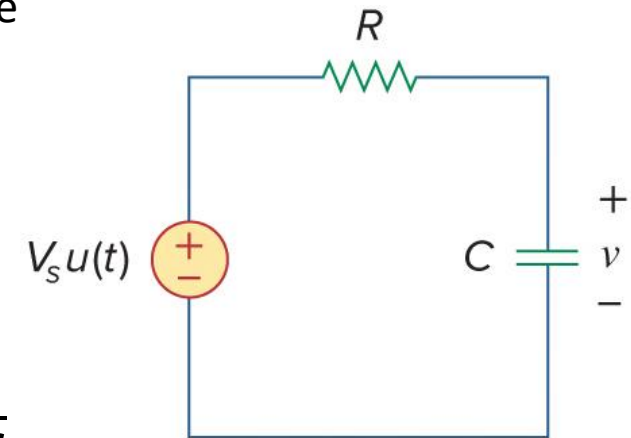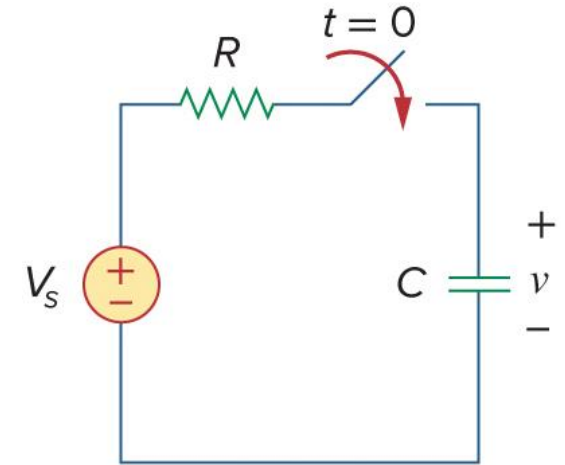
$$\ln(v(t) - V_s) - \ln(V_0 - V_s) = -\frac{t}{RC} + 0 \Rightarrow \ln\left(\frac{v(t) - V_s}{V_0 - V_s}\right) = -\frac{t}{RC}$$



Step Response of an RC Circuit

$$\frac{v(t) - V_s}{V_0 - V_s} = e^{-\frac{t}{RC}} \quad \Rightarrow \quad v(t) - V_s = (V_0 - V_s)e^{-\frac{t}{RC}} \quad \tau = RC$$

$$v(t) = V_s + (V_0 - V_s)e^{-\frac{t}{\tau}} \quad t > 0$$


Complete response (or total response) of the RC circuit to a sudden application of dc voltage source

$$v(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-\frac{t}{\tau}} & t > 0 \end{cases}$$

Assuming capacitor is initially charged

Step Response of an RC Circuit

Assume $V_s > V_0$

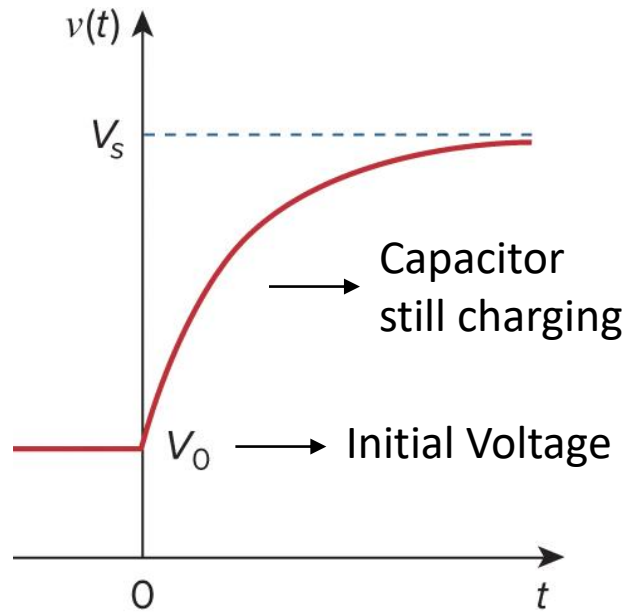

$$v(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-\frac{t}{\tau}} & t > 0 \end{cases}$$

If capacitor is initially uncharged, $V_0 = 0$

$$v(t) = \begin{cases} 0 & t < 0 \\ V_s(1 - e^{-\frac{t}{\tau}}) & t > 0 \end{cases}$$

When $t < 0$, $u(t) = 0$
When $t > 0$, $u(t) = 1$

$$v(t) = V_s(1 - e^{-\frac{t}{\tau}})u(t)$$


Step Response of an RC Circuit

- Current through the capacitor (capacitor initially uncharged):


$$i(t) = C \frac{dv}{dt} = C \frac{d}{dt} \left(V_s (1 - e^{-\frac{t}{\tau}}) \right) \rightarrow i(t) = C \frac{1}{\tau} V_s e^{-\frac{t}{\tau}} \quad \tau = RC \quad t > 0$$

$$i(t) = C \frac{1}{RC} V_s e^{-\frac{t}{\tau}} \rightarrow i(t) = \frac{V_s}{R} e^{-\frac{t}{\tau}} u(t)$$

Capacitor voltage $v(t)$

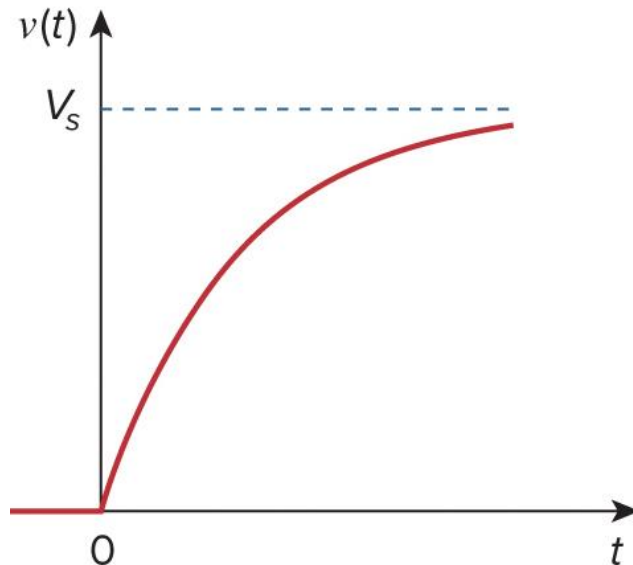

Capacitor current $i(t)$

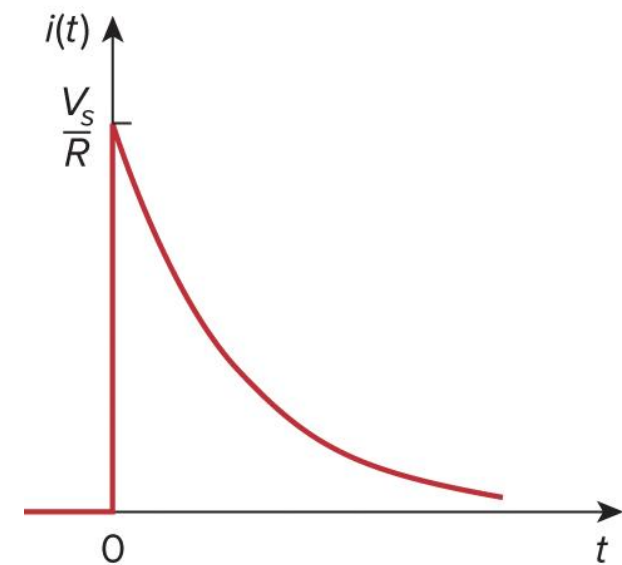

Step Response of an RC Circuit

- Another way of finding step response of an RC & RL circuits.

$$v(t) = V_s + (V_0 - V_s)e^{-\frac{t}{\tau}} \quad \Rightarrow \quad v(t) = V_s + V_0e^{-\frac{t}{\tau}} - V_se^{-\frac{t}{\tau}}$$

$$v(t) = V_0e^{-\frac{t}{\tau}} + V_s(1 - e^{-\frac{t}{\tau}}) \quad \Rightarrow \quad v(t): \text{two components}$$

- Two ways of decomposing into two components:
 - Natural response and forced response
 - Transient response and steady-state response

Step Response of an RC Circuit

- **1st: Natural response and forced response:**
 - Total response or complete response can be written as:

Complete response = natural response + forced response
 (Storage energy) (Independent source)

$$v = v_n + v_f$$

v_n : natural response
 v_f : forced response

$v_n = V_0 e^{-\frac{t}{\tau}}$
➡
 Storage energy

$v_f = V_s (1 - e^{-\frac{t}{\tau}})$
➡
 Independent source

- v_n is the natural response that is produced by capacitor.
- v_f is the forced response that is produced by the circuit when external force (a voltage source) is applied.
- Natural response dies out and leaving only the steady-state component of forced response since as time increases, the capacitor stored energy decreases.

Step Response of an RC Circuit

- **2nd: Transient response and steady-state response:**
 - Total response or complete response can be written as:

Complete response = transient response + steady-state response
 (Temporary part) (Permanent part)

$$v = v_t + v_{ss}$$

v_t : transient response	$v_t = (V_0 - V_s)e^{-\frac{t}{\tau}}$	→ Temporary part
v_{ss} : steady-state response	$v_{ss} = V_s$	→ Permanent part

- Transient response v_t is temporary and decay to zero as time approaches infinity.
- The steady-state response v_{ss} remains after the transient response has die out.

Step Response of an RC Circuit

- The complete response of the general equation may be written as:

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}$$

- $v(0)$: initial voltage
- $v(\infty)$: final or steady-state value.
- Step response of an RC circuit requires three parameters:
 - The initial capacitor voltage $v(0)$
 - The final capacitor voltage $v(\infty)$
 - The time constant τ
- If the switch changes position at time $t = t_0$ instead of $t = 0$, there is a time delay in the response and the equation becomes:

$$v(t) = v(\infty) + [v(t_0) - v(\infty)]e^{-\frac{t-t_0}{\tau}} \quad v(t_0): \text{initial voltage value at } t = t_0$$

Example 6

The switch in the circuit shown below has been in position A for a long time. At $t = 0$, the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 1$ s and $t = 4$ s.

Solution:

For $t < 0$, the switch is at position A. The capacitor acts like an open circuit to dc

$$v(0^-) = \frac{5}{5 + 3}(24) = 15 \text{ V}$$


Capacitor voltage cannot change instantaneously

$$v(0) = v(0^-) = v(0^+) = 15 \text{ V}$$

For $t > 0$, the switch is at position B. Thevenin resistance (equivalent resistance): $R_{Th} = 4 \text{ k}\Omega$

$$\tau = R_{Th}C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ s}$$

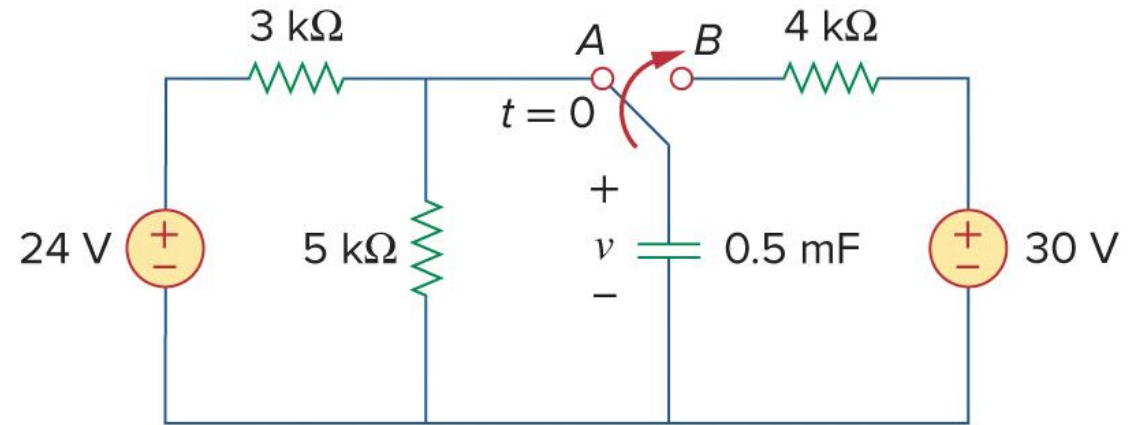Capacitor acts like an open circuit to dc at steady-state, $v(\infty) = 30 \text{ V}$



Complete response:

$$\begin{aligned} v(t) &= v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} \\ &= 30 + (15 - 30)e^{-t/2} = (30 - 15e^{-0.5t}) \text{ V} \end{aligned}$$

$$\text{At } t = 1, \quad v(1) = 30 - 15e^{-0.5} = 20.9 \text{ V}$$

$$\text{At } t = 4, \quad v(4) = 30 - 15e^{-2} = 27.97 \text{ V}$$


Example 7

In the circuit shown below, the switch has been closed for a long time and is opened at $t = 0$. Find i and v for all time.

Solution:

By definition of the unit step function:
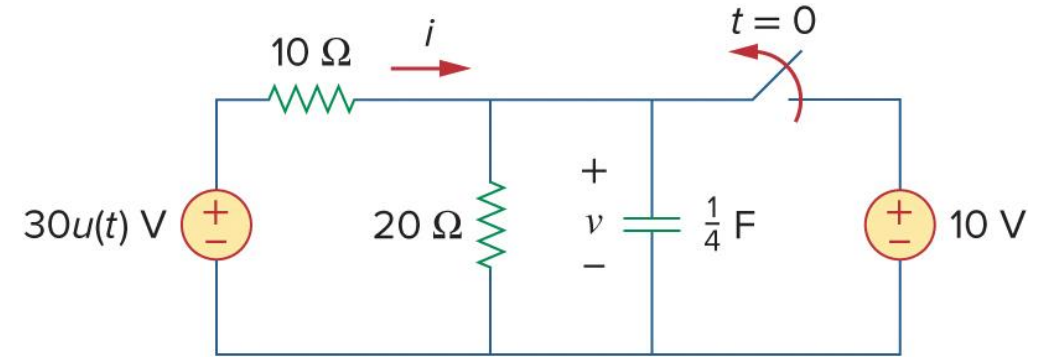
$$30u(t) = \begin{cases} 0 & t < 0 \\ 30 & t > 0 \end{cases} \quad \begin{aligned} v &= 10 \text{ V} \\ i &= -\frac{v}{10} = -1 \text{ A} \end{aligned}$$





$$v(0) = v(0^-) = 10 \text{ V}$$

$$v(\infty) = \frac{20}{20 + 10}(30) = 20 \text{ V} \quad R_{Th} = 10 \parallel 20 = \frac{10 \times 20}{30} = \frac{20}{3} \Omega$$

$$\tau = R_{Th}C = \frac{20}{3} \cdot \frac{1}{4} = \frac{5}{3} \text{ s} \quad \begin{aligned} v(t) &= v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} \\ &= 20 + (10 - 20)e^{-(3/5)t} = (20 - 10e^{-0.6t}) \text{ V} \end{aligned}$$
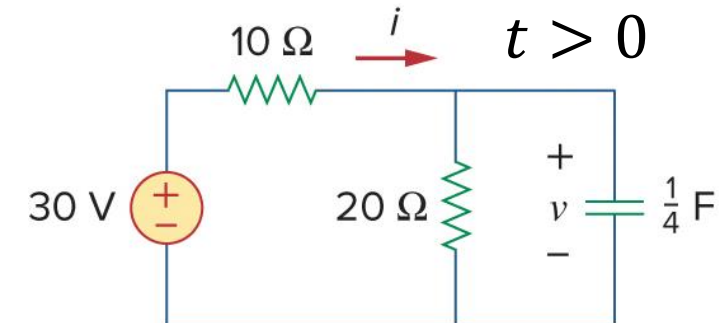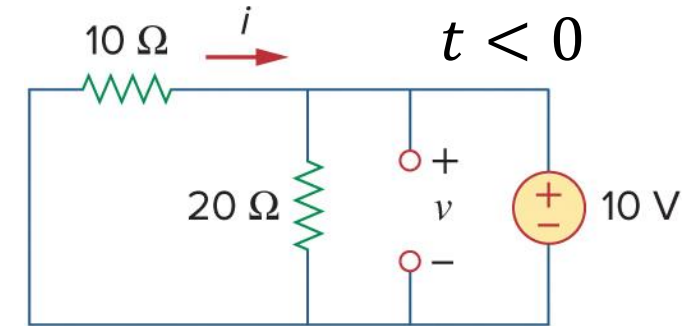
$$i = \frac{v}{20} + C \frac{dv}{dt} = 1 - 0.5e^{-0.6t} + 0.25(-0.6)(-10)e^{-0.6t} = (1 + e^{-0.6t}) \text{ A}$$





Step Response of an RL circuit

- When the switch is closed, there is a sudden of voltage source is applied and the circuit is replaced by the following circuit (on the right)
- The voltage source (or current source) can be modeled as a step function (aka step response).
- Let the current response is sum of transient and steady-state response

$$i = i_t + i_{ss} \quad i_t = Ae^{-\frac{t}{\tau}} \quad \tau = \frac{L}{R} \quad i_{ss} = \frac{V_s}{R} \quad i = Ae^{-\frac{t}{\tau}} + \frac{V_s}{R}$$

- Current through inductor cannot change instantaneously: $i(0^+) = i(0^-) = I_0$
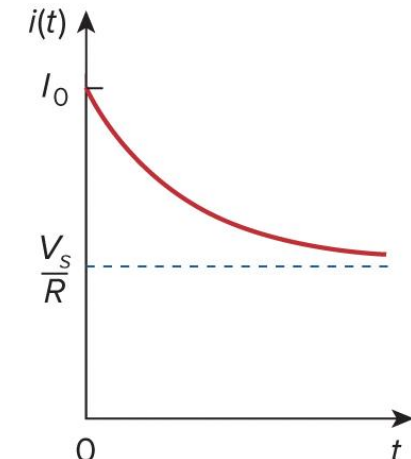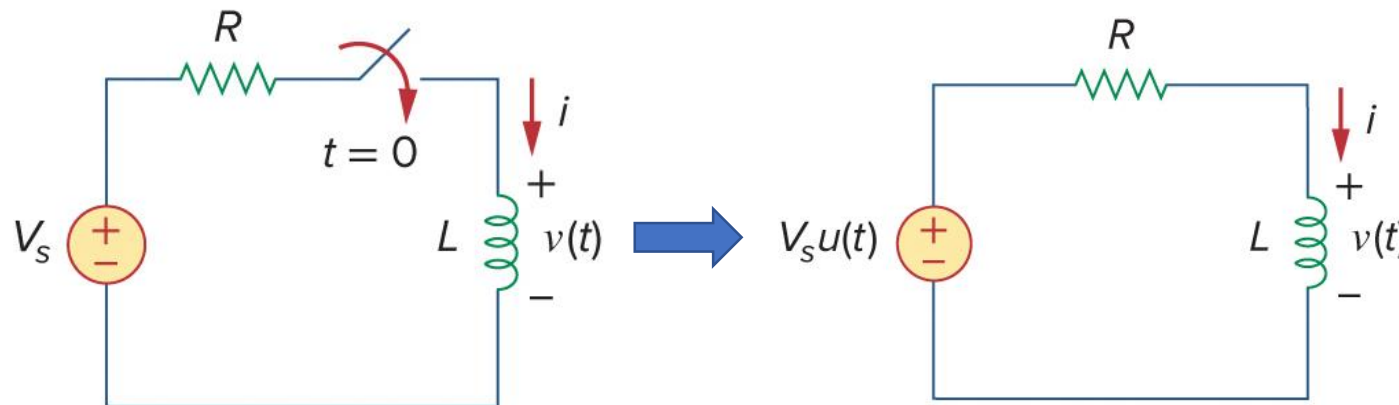
$$\text{At } t = 0, \quad I_0 = A + \frac{V_s}{R} \quad \Rightarrow \quad A = I_0 - \frac{V_s}{R} \quad i(t) = \frac{V_s}{R} + (I_0 - \frac{V_s}{R})e^{-\frac{t}{\tau}}$$



Step Response of an RL circuit



- To find the complete response, RL circuit requires three parameters:
 - The initial inductor current $i(0)$
 - The final inductor current $i(\infty)$
 - The time constant τ

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}} \quad \text{Complete response}$$

$$\text{If } I_0 = 0, \quad i(t) = \begin{cases} 0 & t < 0 \\ \frac{V_s}{R}(1 - e^{-\frac{t}{\tau}}) & t > 0 \end{cases}$$

$$\left. \begin{array}{l} \text{When } t < 0, u(t) = 0 \\ \text{When } t > 0, u(t) = 1 \end{array} \right\} i(t) = \frac{V_s}{R}(1 - e^{-\frac{t}{\tau}})u(t)$$

$$v(t) = L \frac{di}{dt} \Rightarrow v(t) = V_s e^{-\frac{t}{\tau}} u(t)$$

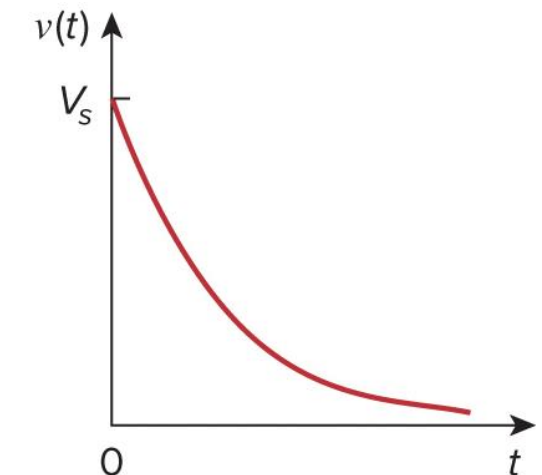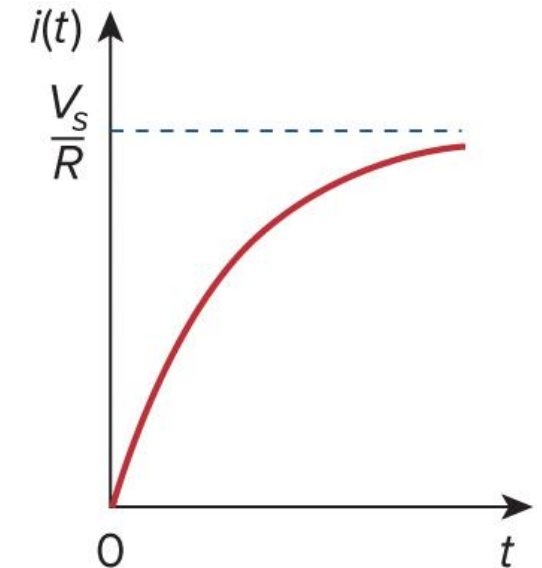

Example 8

Find $i(t)$ in the circuit of shown below for $t > 0$. Assume that the switch has been closed for a long time.

Solution:

When $t < 0$, $3\ \Omega$ resistor is short-circuited and inductor acts like short circuit (dc condition)


$$i(0^-) = \frac{10}{2} = 5\text{ A} \quad i(0) = i(0^+) = i(0^-) = 5\text{ A}$$

$$\text{When } t > 0, \quad i(\infty) = \frac{10}{2 + 3} = 2\text{ A}$$

$$R_{Th} = 2 + 3 = 5\ \Omega \quad \tau = \frac{L}{R_{Th}} = \frac{\frac{1}{3}}{5} = \frac{1}{15}\text{ s}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$= 2 + (5 - 2)e^{-15t} = 2 + 3e^{-15t}\text{ A}, \quad t > 0$$

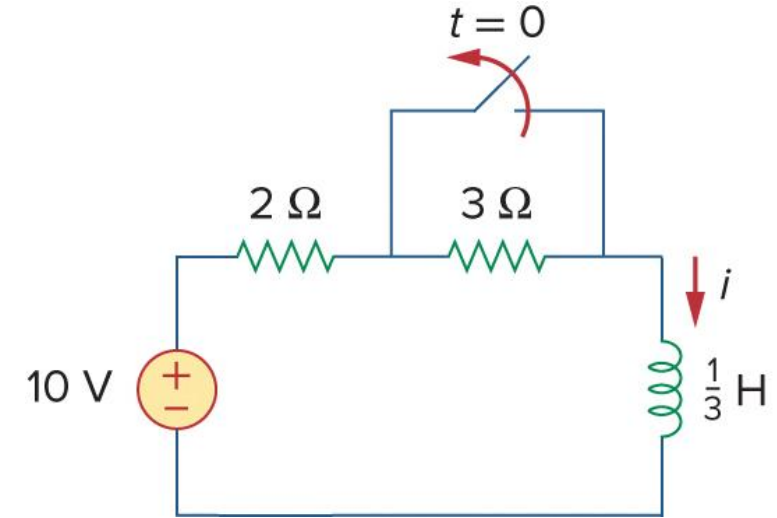

Example 9

- At $t = 0$, switch 1 in the circuit below is closed, and switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2$ s and $t = 5$ s.

Solution:

For $t < 0$, switches S_1 and S_2 are open so that $i = 0$.

$$i(0^-) = i(0) = i(0^+) = 0$$


For $0 \leq t \leq 4$, S_1 is closed $i(\infty) = \frac{40}{4 + 6} = 4$ A,

$$R_{Th} = 4 + 6 = 10 \Omega \quad \tau = \frac{L}{R_{Th}} = \frac{5}{10} = \frac{1}{2} \text{ s}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} = 4 + (0 - 4)e^{-2t} = 4(1 - e^{-2t}) \text{ A}, \quad 0 \leq t \leq 4$$

For $t \geq 4$, S_2 is closed $i(4) = i(4^-) = 4(1 - e^{-8}) \simeq 4$ A
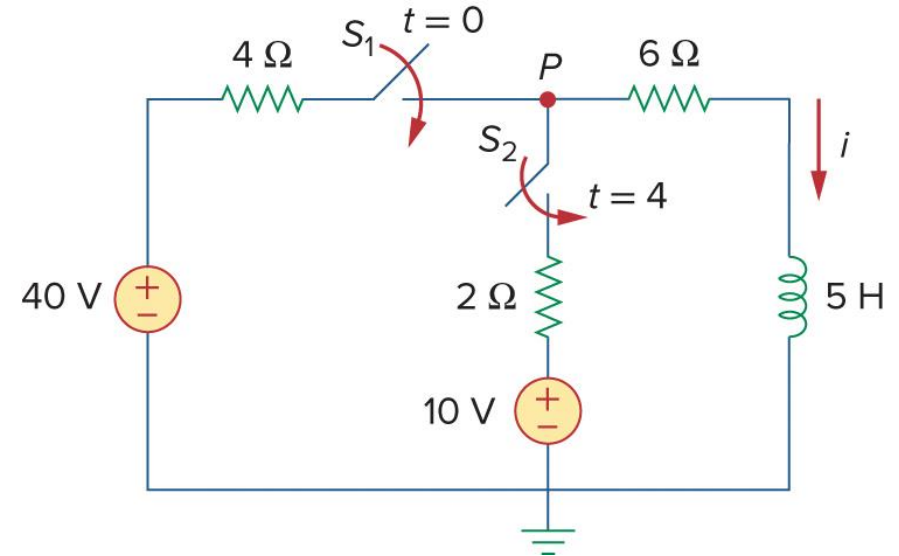
$$\text{Using KCL, } \frac{40 - v}{4} + \frac{10 - v}{2} = \frac{v}{6} \Rightarrow v = \frac{180}{11} \text{ V} \quad i(\infty) = \frac{v}{6} = \frac{30}{11} = 2.727 \text{ A}$$



Solution

$$R_{Th} = 4 \parallel 2 + 6 = \frac{4 \times 2}{6} + 6 = \frac{22}{3} \Omega \quad \tau = \frac{L}{R_{Th}} = \frac{5}{\frac{22}{3}} = \frac{15}{22} \text{ s}$$

$$i(t) = i(\infty) + [i(4) - i(\infty)]e^{-(t-4)/\tau}, \quad t \geq 4$$


$$i(t) = 2.727 + (4 - 2.727)e^{-(t-4)/\tau}, \quad \tau = \frac{15}{22}$$

$$= 2.727 + 1.273e^{-1.4667(t-4)}, \quad t \geq 4$$

$$i(t) = \begin{cases} 0, & t \leq 0 \\ 4(1 - e^{-2t}), & 0 \leq t \leq 4 \\ 2.727 + 1.273e^{-1.4667(t-4)}, & t \geq 4 \end{cases}$$

$$\text{At } t = 2, \quad i(2) = 4(1 - e^{-4}) = 3.93 \text{ A}$$
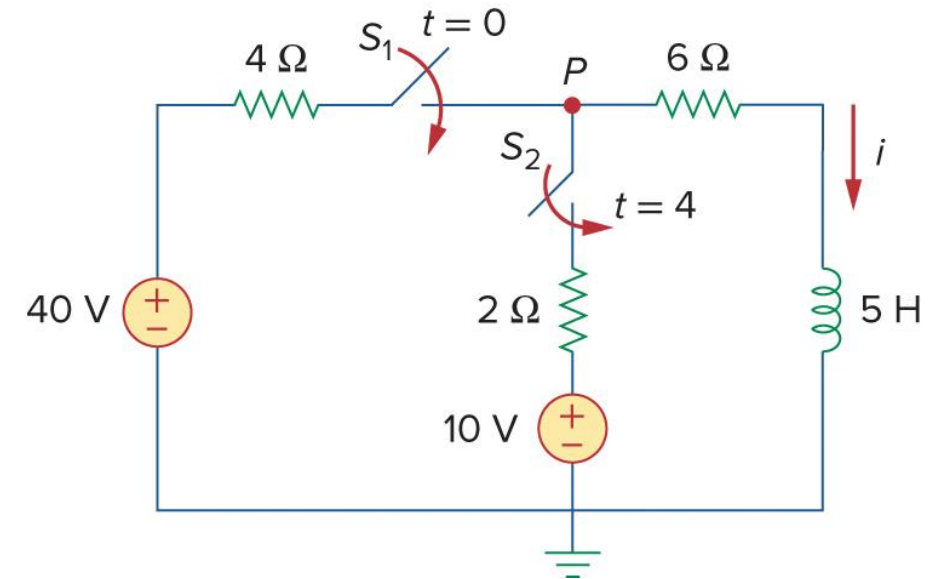
$$\text{At } t = 5, \quad i(5) = 2.727 + 1.273e^{-1.4667} = 3.02 \text{ A}$$



First-Order Op Amp Circuit: Example 10

For the op amp circuit shown below, find v_o for $t > 0$, given that $v(0) = 3 \text{ V}$. Let $R_f = 80 \text{ k}\Omega$, $R_1 = 20 \text{ k}\Omega$, and $C = 5 \mu\text{F}$.

Solution:

Method 1: KCL at node 1: $\frac{0 - v_1}{R_1} = C \frac{dv}{dt}$


$$v_1 = v \quad \frac{dv}{dt} + \frac{v}{CR_1} = 0 \quad \text{Same equation as source free RC}$$

$$v(t) = V_0 e^{-t/\tau}, \quad \tau = R_1 C \quad v(0) = 3 = V_0$$

$$\tau = 20 \times 10^3 \times 5 \times 10^{-6} = 0.1 \quad v(t) = 3e^{-10t}$$

$$\text{Applying KCL at node 2 gives } C \frac{dv}{dt} = \frac{0 - v_o}{R_f} \quad v_o = -R_f C \frac{dv}{dt}$$
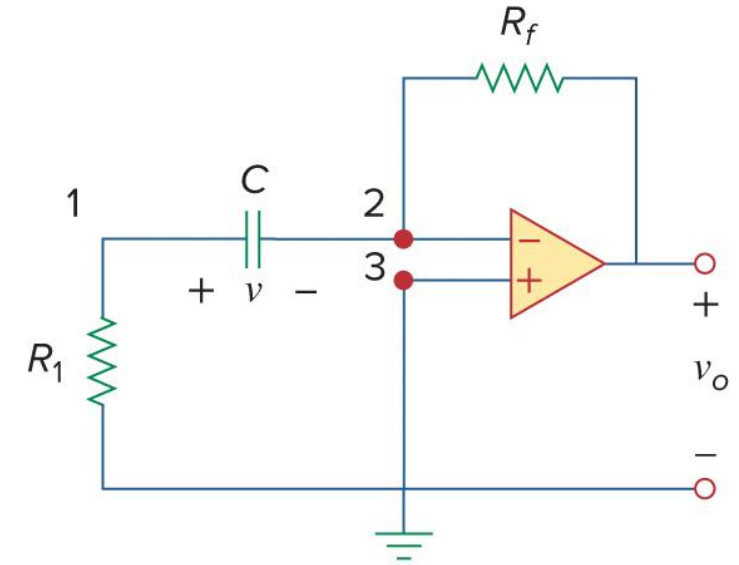
$$v_o = -80 \times 10^3 \times 5 \times 10^{-6} (-30e^{-10t}) = 12e^{-10t} \text{ V}, \quad t > 0$$



Solution

Method 2: $v(0^+) = v(0^-) = 3 \text{ V}$,

apply KCL at node 2
$$\frac{3}{20,000} + \frac{0 - v_o(0^+)}{80,000} = 0 \quad v_o(0^+) = 12 \text{ V}.$$



Since the circuit is source free, $v(\infty) = 0 \text{ V}$.

To find τ , we need to find R_{eq} . Remove capacitor and place 1 A current source (source free circuit). Apply KVL to the input loop:

$$20,000(1) - v = 0 \quad \Rightarrow \quad v = 20 \text{ kV}$$

$$R_{eq} = \frac{v}{1} = 20 \text{ k}\Omega \quad \tau = R_{eq}C = 0.1.$$

$$\begin{aligned} v_o(t) &= v_o(\infty) + [v_o(0) - v_o(\infty)]e^{-t/\tau} \\ &= 0 + (12 - 0)e^{-10t} = 12e^{-10t} \text{ V}, \quad t > 0 \end{aligned}$$

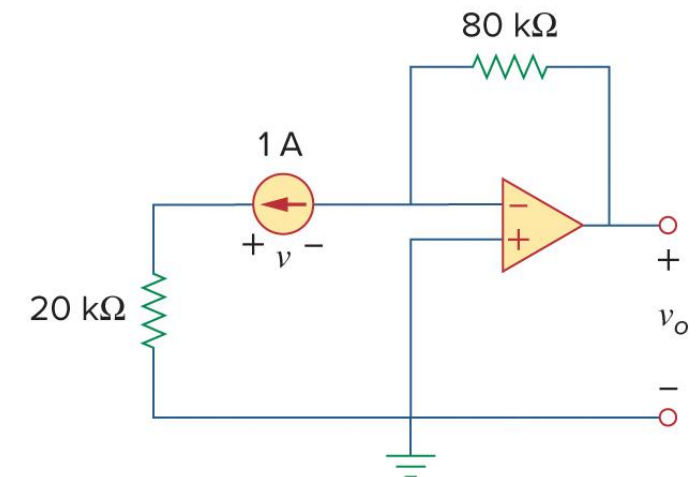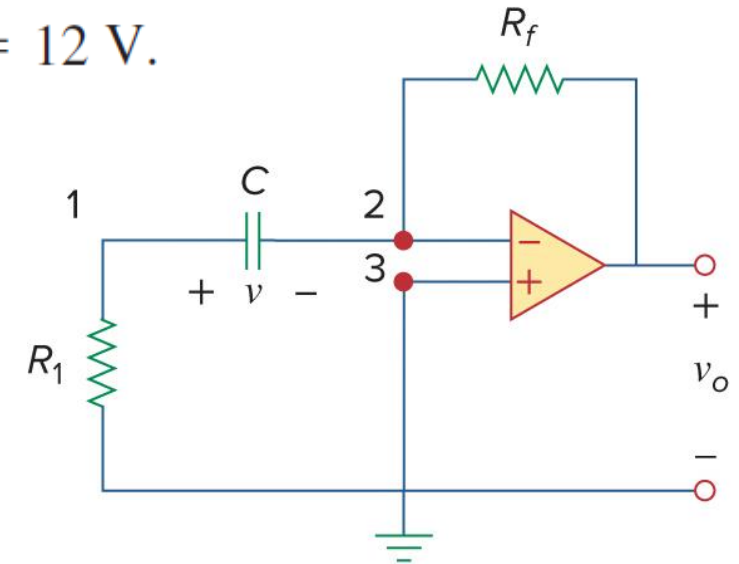

Example 11

Determine $v(t)$ and $v_0(t)$ in the circuit shown below.

Solution:

Since we will find step response, we can write the following equation:

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}, \quad t > 0$$

$$\tau = RC = 50 \times 10^3 \times 10^{-6} = 0.05$$

$t < 0$, the switch is open and no voltage across capacitor
 $v(0) = 0$.


$$t > 0, \quad v_1 = \frac{20}{20 + 10} 3 = 2 \text{ V}$$

$$v_o(\infty) = \left(1 + \frac{50}{20}\right)v_1 = 3.5 \times 2 = 7 \text{ V}$$

$$v_1 - v_o = v \quad v(\infty) = 2 - 7 = -5 \text{ V}$$

$$v(t) = -5 + [0 - (-5)]e^{-20t} = 5(e^{-20t} - 1) \text{ V}, \quad t > 0$$
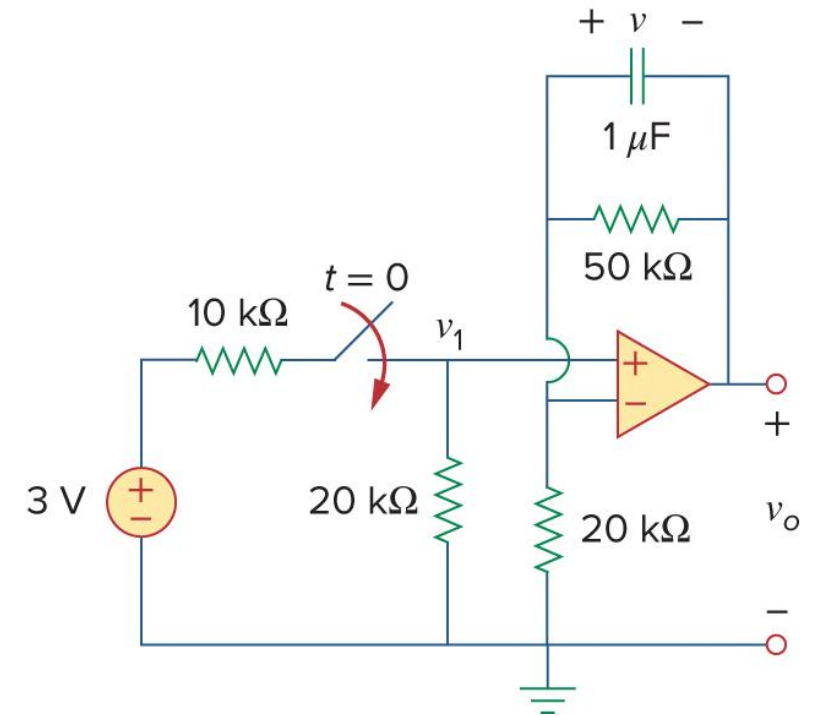
$$v_o(t) = v_1(t) - v(t) = 7 - 5e^{-20t} \text{ V}, \quad t > 0$$



Capacitor acts like an open circuit to dc and op amp circuit behaves like an noninverting op amp.

Noninverting op amp:

$$v_o = \left(1 + \frac{R_f}{R_1}\right)v_1$$

Example 12

Find the step response $v_o(t)$ for $t > 0$ in the op amp circuit shown below. Let $v_i = 2u(t)$ V, $R_1 = 20$ k Ω , $R_f = 50$ k Ω , $R_2 = R_3 = 10$ k Ω , and $C = 2$ μ F.

Solution:

Using Thevenin theorem may simplify the example. Remove the capacitor and find the Thevenin equivalent circuit

$$V_{ab} = -\frac{R_f}{R_1}v_i \quad V_{Th} = \frac{R_3}{R_2 + R_3}V_{ab} = -\frac{R_3}{R_2 + R_3}\frac{R_f}{R_1}v_i$$

$$V_{Th} = -\frac{R_3}{R_2 + R_3}\frac{R_f}{R_1}v_i = -\frac{10}{20 + 10}\frac{50}{20}2u(t) = -2.5u(t)$$

$$R_{Th} = \frac{R_2 R_3}{R_2 + R_3} = 5 \text{ k}\Omega \quad \longrightarrow \quad R_{Th} \text{ can be found by turning off the input voltage } v_i. \text{ Doing so, } v_{ab} \text{ will be zero}$$

$$v_o(t) = -2.5(1 - e^{-t/\tau})u(t)$$

$$\tau = R_{Th}C = 5 \times 10^3 \times 2 \times 10^{-6} = 0.01$$

$$v_o(t) = 2.5(e^{-100t} - 1)u(t) \text{ V}$$

