

**Instructor:**

Asst. Prof. Onur Kurt

**Student Name:**

**ID:**

**Date:**

**ITU**

**EEB 211E: Basics of Electrical Circuits (Fall 2020)**

**Homework #1**

**Grading Policy:**


- You must upload your homework assignment to Ninova before its due date. Late homework will not be accepted/graded.
- Homework should be written clearly and legibly. Your answers should show step-by-step solution of each question. Messy and illegible homework may not be graded.
- You must not ask for answers directly from any aide.
- Academic dishonesty is unacceptable. Plagiarism and cheating on the homework assignment will result in a zero grade.

**Question 1-)** Find the current flowing through an element if the charge flow is given by


(a)  $q(t) = (2e^{-t} - 4e^{-3t}) \text{ nC}$

(b)  $q(t) = 30\cos(100\pi t) \text{ pC}$


**Question 2-**) The charge flowing in a conducting wire is plotted in the figure shown below. Sketch graph of the corresponding current.

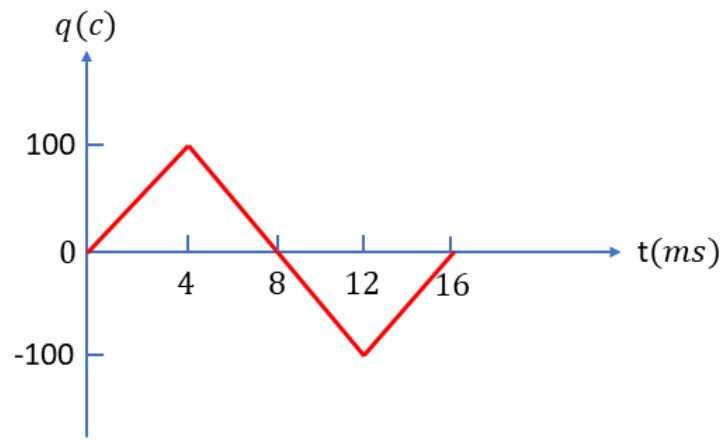


**Question 3-** Calculate the power supplied or absorbed by each element in the figure shown below and verify Tellegen's theorem.

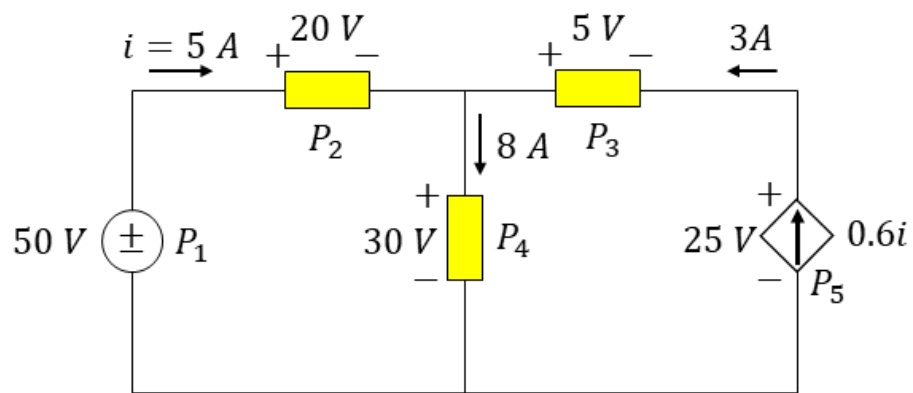

**Question 4-** For the circuit shown below, find  $i_a$ ,  $i_b$ ,  $i_c$ ,  $v_x$  and the power dissipated in the 50- $\Omega$  resistor.

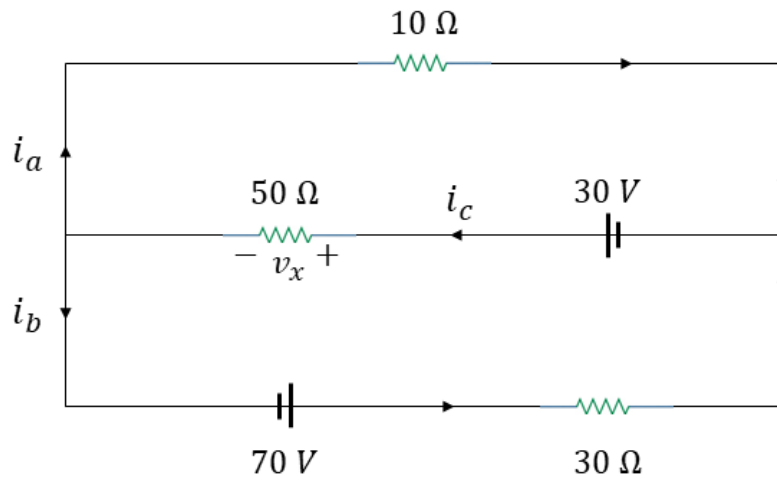

**Question 5-** For the circuit shown below, obtain the equivalent resistance  $R_{eq}$  and use it to find current  $i_0$ .

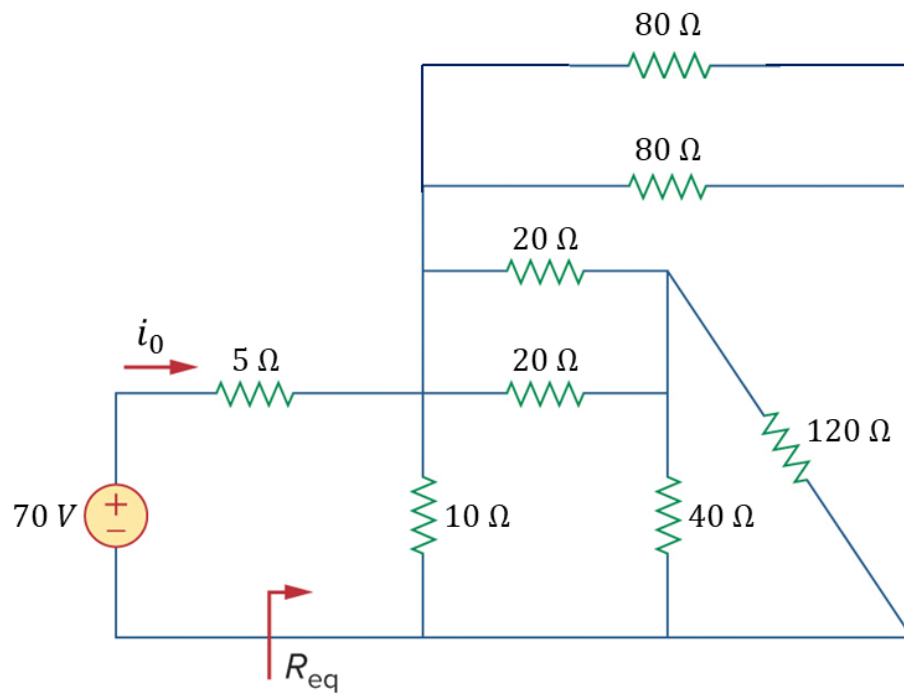

**Question 6-** Find the current  $i_0$  in the circuit shown below.

